 


Example :Configuring LUT

- LUT is a RAM with data width of 1bit.
- The contents are programmed at power up


Required Function



Truth Table

a	b	c	y
0	0	0	1
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

Programmed LUT

 


FPGA Principles


- A Field-Programmable Gate Array (FPGA) is an integrated circuit that can be configured by the user to emulate any digital circuit as long as there are enough resources
- An FPGA can be seen as an array of Configurable Logic Blocks (CLBs) connected through programmable interconnect (Switch Boxes)



Comparison

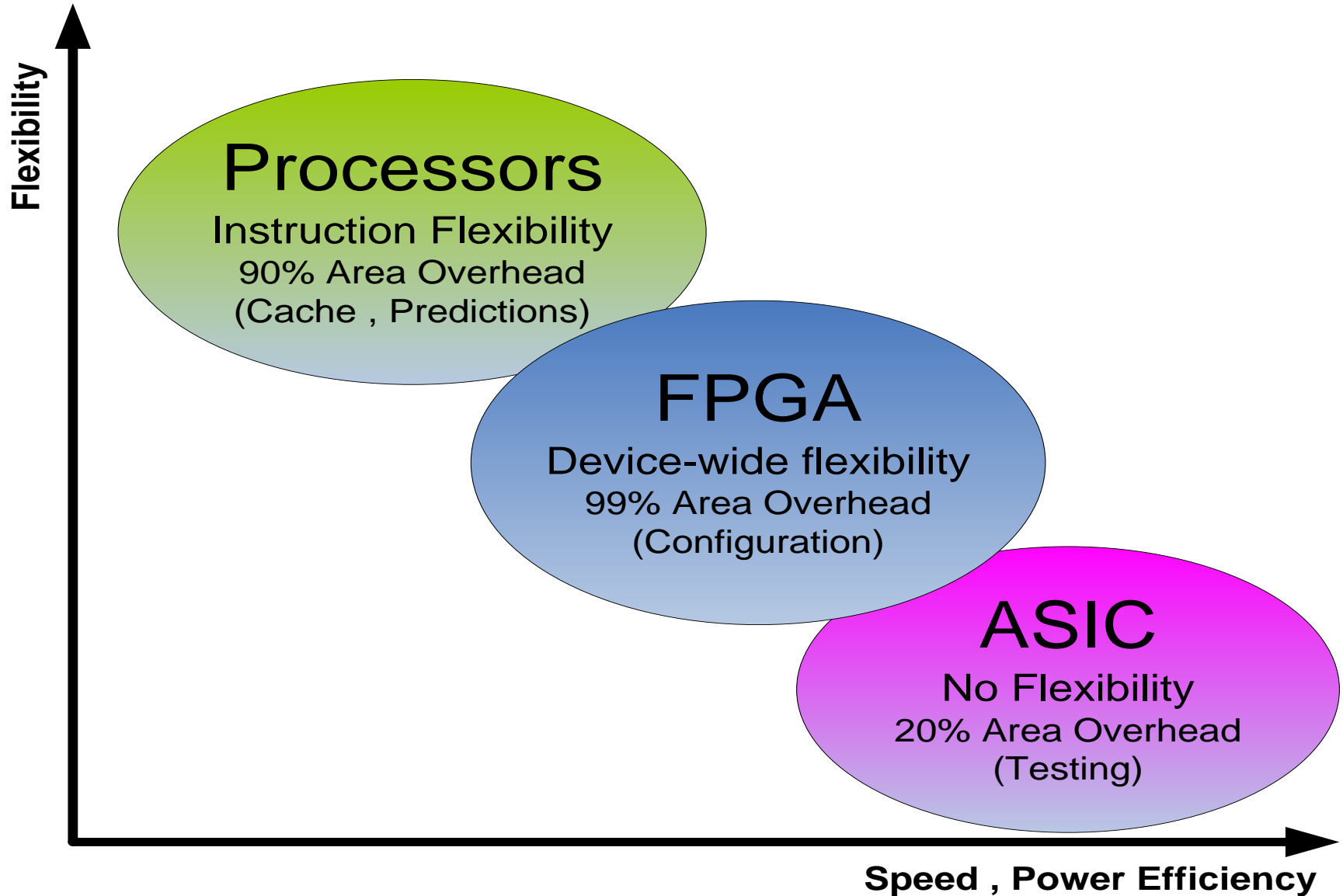

Xilinx Spartan-3E Starter Kit


 


Logic Arrays


- Programmable logic arrays (PLAs)
 - AND array followed by OR array
 - Perform combinational logic only
 - Fixed internal connections
- Field programmable gate arrays (FPGAs)
 - Array of configurable logic blocks (CLBs)
 - Perform combinational and sequential logic
 - Programmable internal connections

PLAs

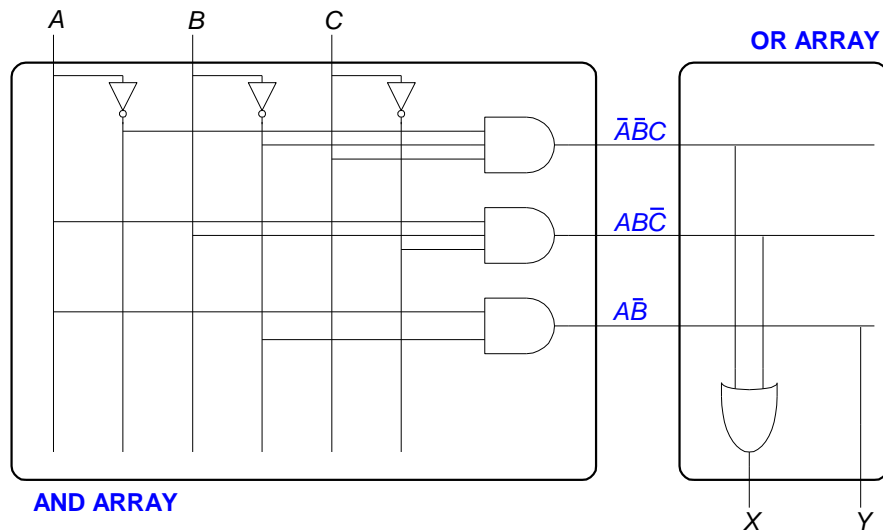 - $X = \bar{A}\bar{B}C + AB\bar{C}$
- $Y = A\bar{B}$




PLAs: Dot Notation

 

FPGAs: Field Programmable Gate Arrays

- Composed of:
 - **CLBs** (Configurable logic blocks): perform logic
 - **IOBs** (Input/output buffers): interface with outside world
 - **Programmable interconnection**: connect CLBs and IOBs
 - Some FPGAs include other building blocks such as multipliers and RAMs

Xilinx Spartan 3 FPGA Schematic

 


D6099-1_01_092703

CLBs: Configurable Logic Blocks

- Composed of:
 - LUTs (lookup tables): perform combinational logic
 - Flip-flops: perform sequential functions
 - Multiplexers: connect LUTs and flip-flops

Xilinx Spartan CLB

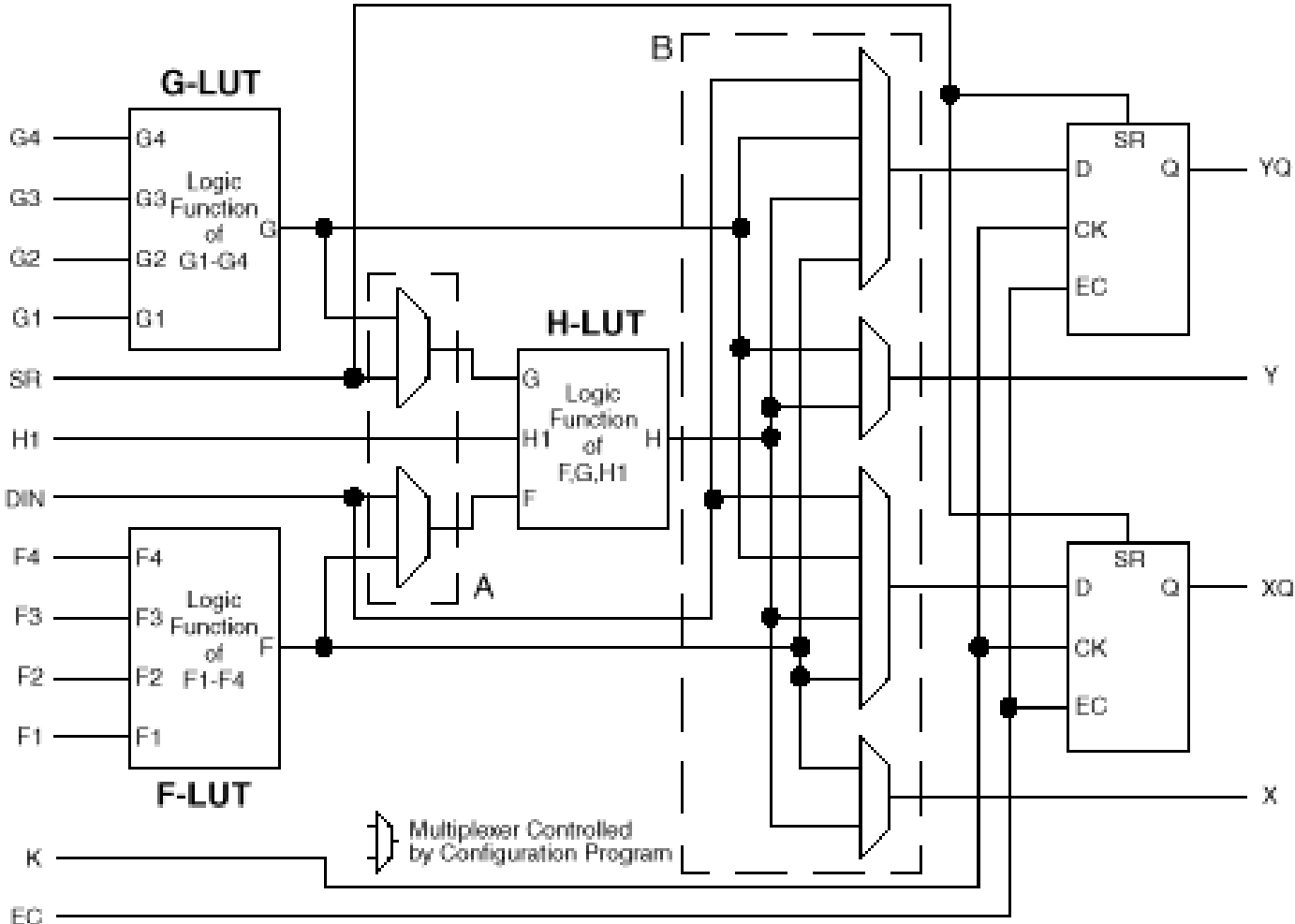


Xilinx Spartan CLB

- The Spartan CLB has:
 - 3 LUTs:
 - F-LUT (2^4 x 1-bit LUT)
 - G-LUT (2^4 x 1-bit LUT)
 - H-LUT (2^3 x 1-bit LUT)
 - 2 registered outputs:
 - XQ
 - YQ
 - 2 combinational outputs:
 - X
 - Y

CLB Configuration Example

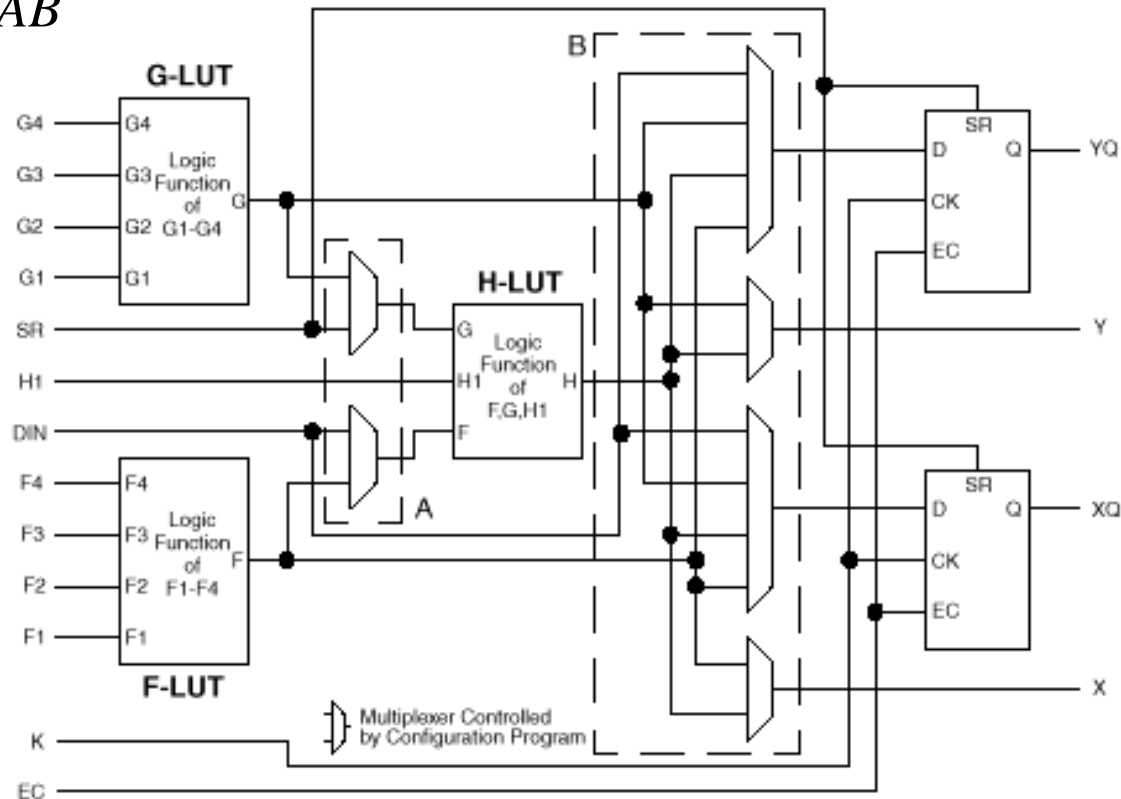- Show how to configure the Spartan CLB to perform the following functions:
 - $X = \overline{A}BC + A\overline{B}C$
 - $Y = A\overline{B}$




CLB Configuration Example

- Show how to configure the Spartan CLB to perform the following functions:
 - $X = \overline{A}\overline{B}C + A\overline{B}\overline{C}$
 - $Y = A\overline{B}$

	(A)	(B)	(C)	(X)
F4	F3	F2	F1	F
X	0	0	0	0
X	0	0	1	1
X	0	1	0	0
X	0	1	1	0
X	1	0	0	0
X	1	0	1	0
X	1	1	0	1
x	1	1	1	0

		(A)	(B)	(Y)
G4	G3	G2	G1	G
X	X	0	0	0
X	X	0	1	0
X	X	1	0	1
X	X	1	1	0

 

FPGA Design Flow


- A CAD tool (such as Xilinx Project Navigator) is used to design and implement a digital system. It is usually an iterative process.
- The user **enters the design** using schematic entry or an HDL(verilog).
- The user **simulates** the design.
- A **synthesis** tool converts the code into hardware and maps it onto the FPGA.
- The user uses the CAD tool to **download the configuration** onto the FPGA
- This configures the CLBs and the connections between them and the IOBs.

Manufacturers


- Xilinx
- Altera
- Lattice
- Actel



FPGA structure

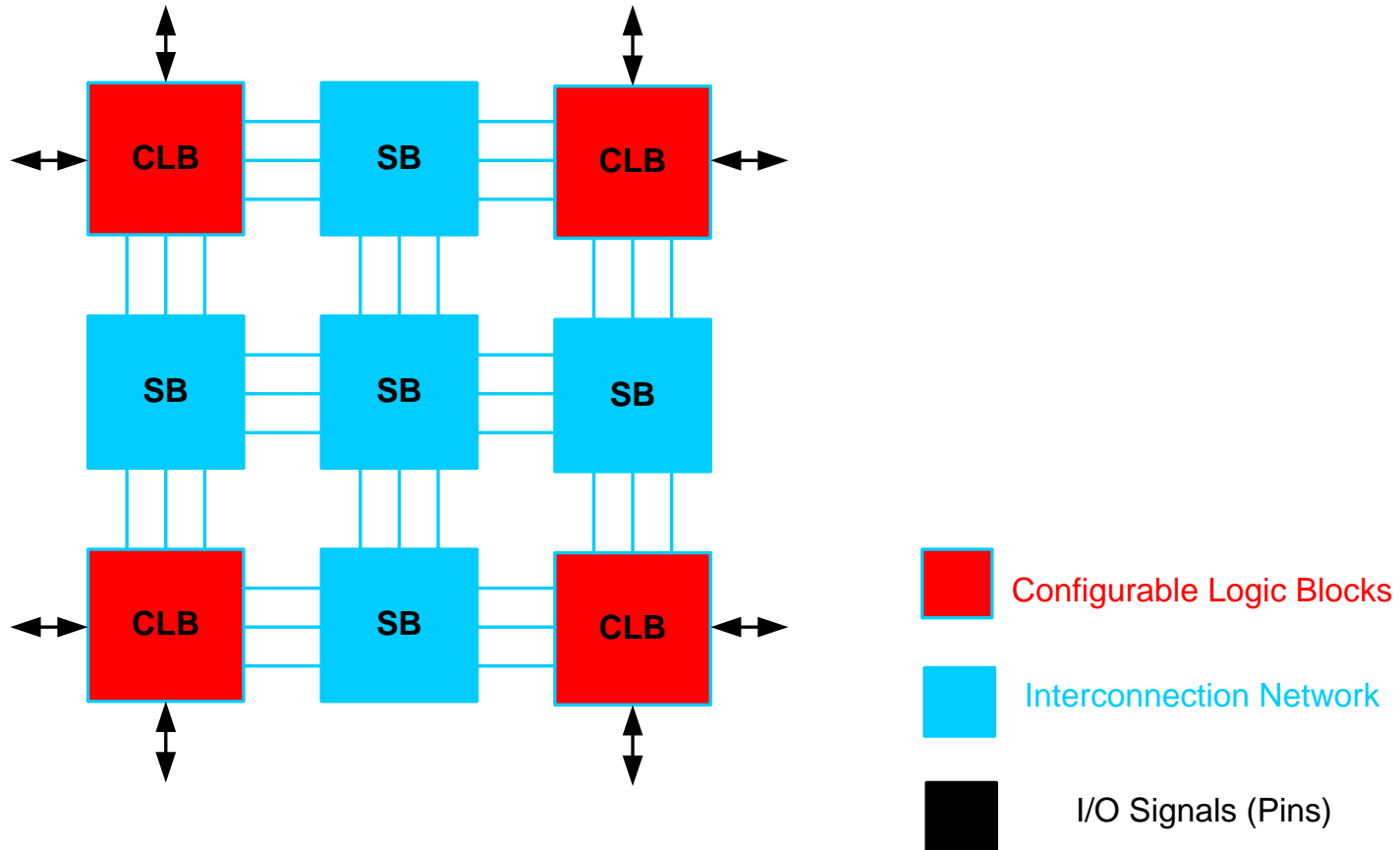

Simplified CLB Structure

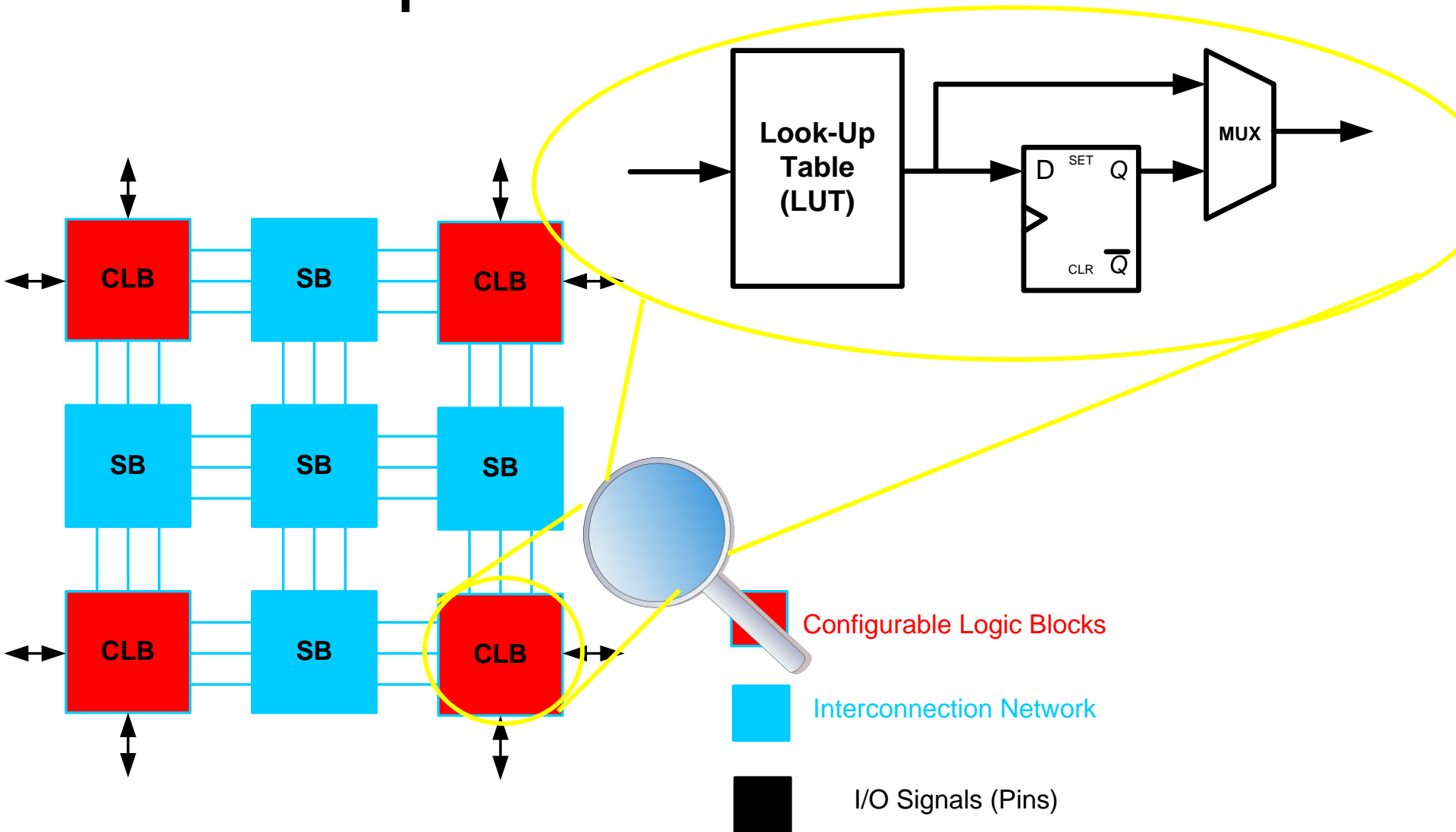

The diagram illustrates a 4-to-1 MUX implementation using a 16-to-1 MUX and a D flip-flop. The 16-to-1 MUX has 16 inputs, all of which are 0, except for the bottom input which is 1. This input vector is labeled "Configuration bits" with a green oval and arrow. The 16-to-1 MUX has four data inputs (A, B, C, D) and one output. The output of the 16-to-1 MUX is connected to the D input of a D flip-flop. The flip-flop also has a SET input (connected to the top input of the 16-to-1 MUX, which is 0), a CLR input (connected to the bottom input of the 16-to-1 MUX, which is 1), and a Q output. The Q output of the flip-flop is connected to the MUX input of a 4-to-1 MUX. The 4-to-1 MUX has four data inputs (A, B, C, D) and one output. The output of the 4-to-1 MUX is 0.