

CS 225 Switching Theory

Dr. Somanath Tripathy
Indian Institute of Technology Patna

Previous Class

Combinational Circuit logic design

This Class

Combinational Circuit logic design

Combinational Logic Design Process





n inputs



Step	Description
Step 1: Capture behavior	<p>Capture the function</p> <p>Create a truth table or equations, <i>whichever is most natural for the given problem</i>, to describe the desired behavior of each output of the combinational logic.</p>
Step 2: Convert to circuit	<p>2A: Create equations</p> <p>2B: Implement as a gate-based circuit</p> <p>This substep is only necessary if you captured the function using a truth table instead of equations. Create an equation for each output by ORing all the minterms for that output. Simplify the equations if desired.</p> <p>For each output, create a circuit corresponding to the output's equation. (Sharing gates among multiple outputs is OK optionally.)</p>

Warmup (NAND/NOR) Circuits

    Switching algebra: not directly applicable to NAND/NOR logic



NAND and NOR gate symbols


Warm-up (Decoders)

Decoders with n inputs and 2^n outputs: for any input combination, only one output is 1

Useful for:

- Routing input data to a specified output line, e.g., in addressing memory
- Basic building blocks for implementing arbitrary switching functions
- Code conversion
- Data distribution

Example: 2-to-4- decoder

 


Warm-up (Decoders)


3-8 line Decoder Truth table

Inputs			Outputs							
x_2	x_1	x_0	z_0	z_1	z_2	z_3	z_4	z_5	z_6	z_7
0	0	0	0	1	1	1	1	1	1	1
0	0	1	1	0	1	1	1	1	1	1
0	1	0	1	1	0	1	1	1	1	1
0	1	1	1	1	1	0	1	1	1	1
1	0	0	1	1	1	1	0	1	1	1
1	0	1	1	1	1	1	1	0	1	1
1	1	0	1	1	1	1	1	1	0	1
1	1	1	1	1	1	1	1	1	1	0

3-8 line Bubbled output Decoder Symbol

 

 3-8 line Decoder using Nand gates Logic Diagram



Generates a single output (desired) low

Warmup (Implementing Boolean expression)

Using Decoder Ex.: Realize using 3x8 decoder

$$f1 = \sum m(1,2,4,5) \text{ and } f2 = \sum m(1,5,7)$$


Realize the above function with given bubbled output decoder (Nand gate decoder)

Warmup (Multiplexer)

Multiplexer: electronic switch that connects one of n inputs to the output

Data selector: application of multiplexer

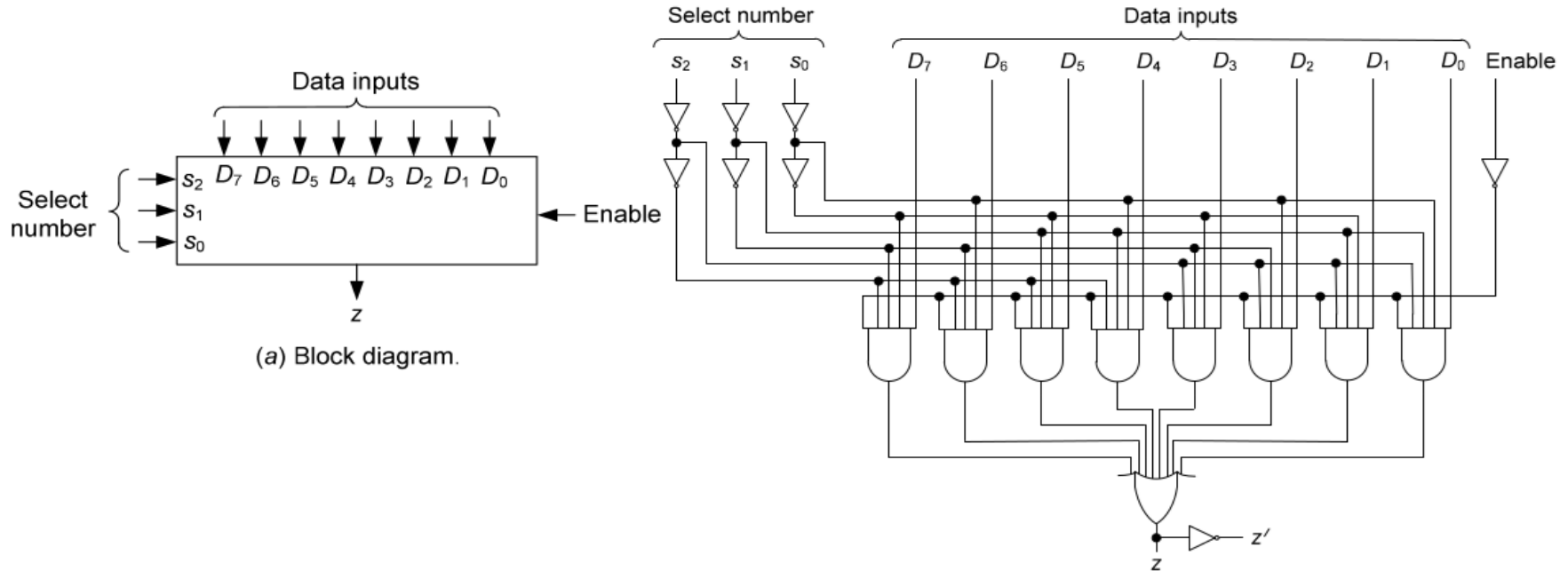- n data input lines, D_0, D_1, \dots, D_{n-1}
- m select digit inputs S_0, S_1, \dots, S_{m-1}
- 1 output



(a) Block diagram.

(b) Logic diagram.

Implementing Boolean expression using

Using Multiplexer Ex.: Realize $F(x,y,z) = \sum m(1,2,6,7)$ using 4x1 Mux

Design of High-speed Adders

Full adder: performs binary addition of three binary digits

- Inputs: arguments A and B and carry-in C
- Outputs: sum S and carry-out C_0


Example:

$$\begin{array}{r}
 0 \ 1 \ 1 \quad = \quad \text{carry-in} \\
 1 \ 0 \ 0 \ 1 \quad = \\
 0 \ 0 \ 1 \ 1 \quad = \\
 \hline
 1 \ 1 \ 1 \ 0 \quad =
 \end{array}
 \begin{array}{l}
 \text{augend} \\
 \text{addend} \\
 \text{sum}
 \end{array}$$

Truth table, block diagram and expressions:

A	B	C	S	C ₀
0	0	0	0	0
0	0	1	1	0
0	1	1	0	1
0	1	0	1	0
1	1	0	0	1
1	1	1	1	1
1	1	1	0	1
1	0	0	1	0
 
$$\begin{aligned}
 S &= A'B'C + A'BC' + AB'C' + ABC \\
 &= A \oplus B \oplus C \\
 C_0 &= A'BC + ABC' + AB'C + ABC \\
 &= AB + AC + BC
 \end{aligned}$$




(b) Block diagram.

Ripple-carry Adder

Ripple-carry adder: Stages of full adders

 - C_f : forced carry
- $C_{0(n-1)}$: overflow carry



$$S_i = A_i \oplus B_i \oplus C_i$$


$$C_{0i} = A_i B_i + A_i C_i + B_i C_i$$

Time required:

- Time per full adder: 2 units
- Time for ripple-carry adder: $2n$ units

Carry Propagation & Delay

 
- One problem with the addition of binary numbers is the length of time to propagate the ripple carry from the least significant bit to the most significant bit.
- The gate-level propagation path for a 4-bit ripple carry adder of the last example:



- Note: The "long path" is from A_0 or B_0 through the circuit to S_3 .

Carry Lookahead

 - Given Stage i from a Full Adder, we know that there will be a carry generated when $A_i = B_i = "1"$, whether or not there is a carry-in.
- Alternately, there will be a carry propagated if the "half-sum" is "1" and a carry-in, C_i occurs.
- These two signal conditions are called *generate*, denoted as G_i , and *propagate*, denoted as P_i respectively and are identified in the circuit:



Carry Lookahead (continued)

- In the ripple carry adder:
 - G_i , P_i , and S_i are local to each cell of the adder
 - C_i is also local each cell
- In the carry lookahead adder, in order to reduce the length of the carry chain, C_i is changed to a more global function spanning multiple cells
- Defining the equations for the Full Adder in term of the P_i and G_i :

$$S_i = P_i \oplus C_i$$

$$C_{i+1} = G_i + P_i C_i$$

$$P_i = A_i \oplus B_i$$

$$G_i = A_i B_i$$

Example - 4-bit Adder


$$c_1 = G_0 + c_0 P_0,$$

$$c_2 = G_1 + G_0 P_1 + c_0 P_0 P_1,$$


$$c_3 = G_2 + G_1 P_2 + G_0 P_1 P_2 + c_0 P_0 P_1 P_2,$$

$$c_4 = G_3 + G_2 P_3 + G_1 P_2 P_3 + G_0 P_1 P_2 P_3 + c_0 P_0 P_1 P_2 P_3$$

A carry lookahead generator.

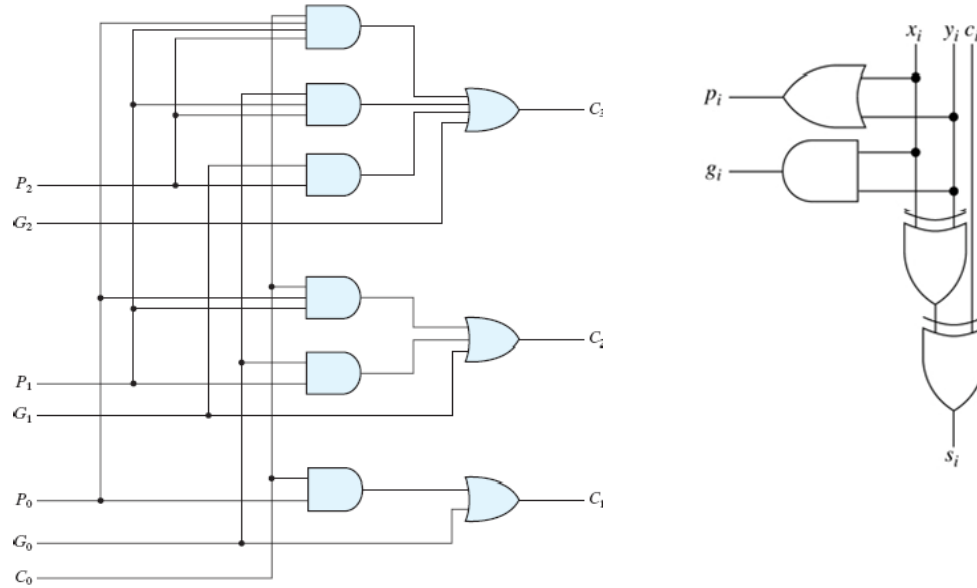

A carry lookahead Adder

 

Thanks

Wish you all have a Good Exam