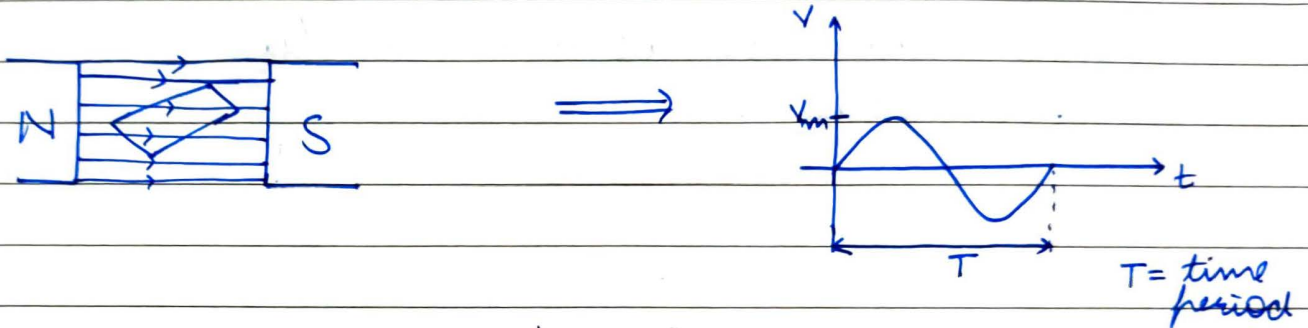


## chapter - AC Analysis

### → PRODUCTION OF AC →

- When a conductor coil is rotated in a magnetic field, a current is produced through it



- We rotate the coil with  $\omega$  angular velocity where  $\omega = 2\pi f = 2\pi/T$

So we can write this wave as

$$V = V_m \sin(\omega t)$$

- Now we find **root mean square voltage**


$$V_{rms} = \sqrt{\frac{1}{T} \int_0^T (V_m \sin \omega t)^2 dt}$$

$$\Rightarrow \boxed{V_{rms} = V_m / \sqrt{2}}$$

NOTE: The voltage displayed in electrical circuits is 250V is actually  $V_{rms}$ .

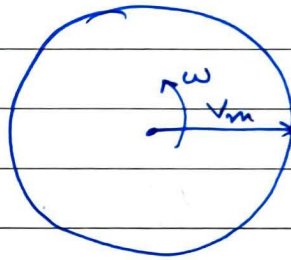
### → REPRESENTATION OF AC →

- We represent voltage ~~vectors~~ as a rotating phasor vector.
- We take anti-clockwise as +ve direction and clockwise as -ve direction by convention



- This phasor vector ~~lies in~~
- We assume this phasor vector to lie in complex plane for ease of calculations

eg-

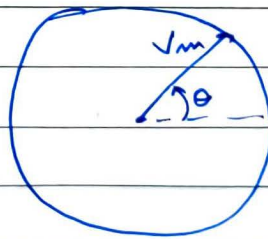

We represent this as  $V_m = V_m \angle \theta$

$$V_m = V_m \angle \theta$$



$$\Rightarrow V = V_m e^{j\theta}$$

$$j = \sqrt{-1}$$

$$\Rightarrow V = V_m \cos \theta + j V_m \sin \theta$$

## → RESISTOR IN AC CIRCUITS →


- now consider

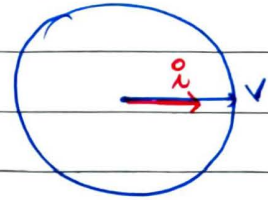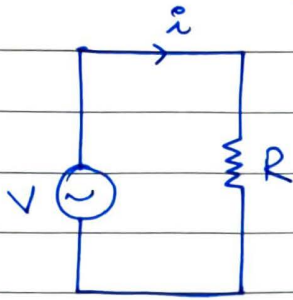


$$i = V/R$$

$$\Rightarrow i = \frac{V_m \sin \omega t}{R}$$


$$\Rightarrow i = I_m \sin \omega t$$

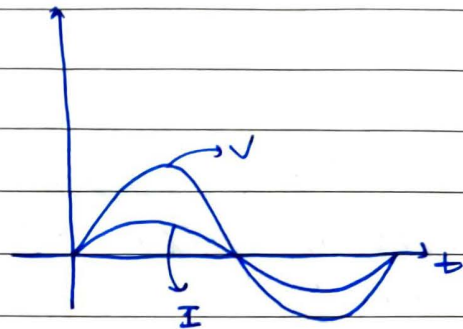

- consider

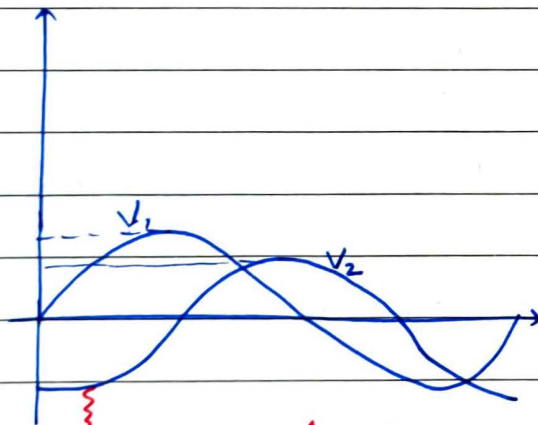

$\Rightarrow$

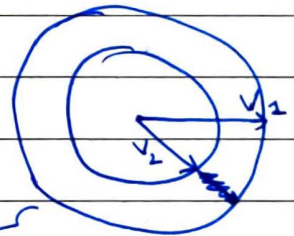

lagging behind and since it's -ve  $\therefore$  it lags behind  
ie in anticlockwise direction



## → IMPEDANCE

- Impedance is defined as


$$Z = \frac{V}{I}$$

- For resistor,  $Z = \frac{V_m \sin \omega t}{I_m \sin \omega t}$

$$\Rightarrow \boxed{Z_R = R}$$

- Impedance can even be complex; what we used to calculate in class 12 was  $|Z|$  i.e. its magnitude.

## → INDUCTOR IN AC CIRCUITS

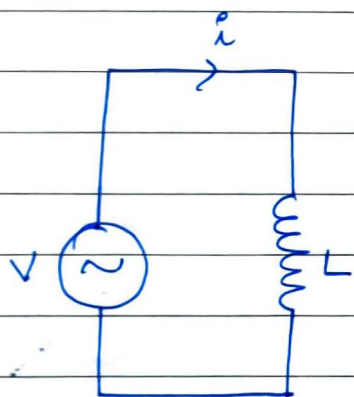

$$V = L \frac{di}{dt} \quad \text{across inductor}$$

$$\Rightarrow L \frac{di}{dt} = V_m \sin \omega t$$

$$\Rightarrow \int di = \frac{V_m}{L} \int \sin \omega t \, dt$$

$$\Rightarrow Li = -\frac{V_m}{\omega} \cos \omega t$$

$$\Rightarrow Li = \frac{V_m}{\omega} \sin(\omega t - \pi/2) \Rightarrow i = \frac{V_m}{\omega L} \sin(\omega t - \pi/2)$$

now,

$$Z = \frac{V}{I} = \frac{V_m \sin \omega t}{(\frac{V_m}{\omega L}) \sin(\omega t - \pi/2)}$$

$$\Rightarrow Z = \frac{\omega L \sin \omega t}{-j \sin \omega t}$$

$$\Rightarrow \boxed{Z_L = j\omega L}$$

Impedance of inductor


$$\begin{array}{l} \sin \omega t \\ \sin(\omega t - \pi/2) \\ \text{or } -j \sin \omega t \end{array}$$

- Here, we also define

$$\boxed{X_L = \omega L}$$

is reactance of inductor

## → CAPACITOR IN AC CIRCUITS

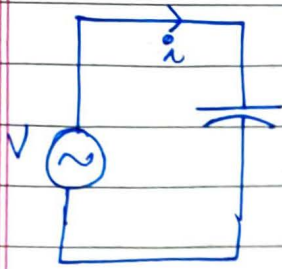

$$i = C \frac{dV}{dt}$$


$$= C \frac{d(V_m \sin \omega t)}{dt}$$

$$\Rightarrow i = CV_m \omega \cos \omega t$$

$$\Rightarrow i = CV_m \omega \sin(\omega t + \pi/2)$$

$$\Rightarrow i = I_m \sin(\omega t + \pi/2)$$

• If represented as a phasor, we get

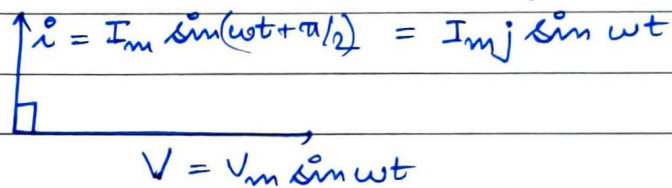

•  $\therefore$  we have

$$i = C \omega V_m j \sin \omega t$$


$$\therefore Z = \frac{V}{I} = \frac{V_m \sin \omega t}{j C \omega V_m \sin \omega t}$$

$$\Rightarrow \boxed{Z_c = \frac{1}{j C \omega}} \rightsquigarrow \text{Impedance of capacitor}$$

• We define

$$\boxed{X_c = \frac{1}{\omega C}}$$

is reactance of capacitor.

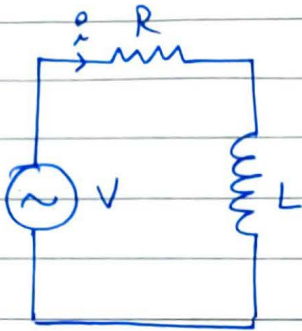→ RL Circuit

Impedance of inductor  $= jX_L$   
 $= j\omega L$

Total Impedance  $Z = R + j\omega L$   
 $|Z| = \sqrt{R^2 + \omega^2 L^2}$

$$\text{KVL} \equiv V = Ri + L \frac{di}{dt}$$

Or we can directly write

$$V = Ri + i j\omega L$$


$$\Rightarrow i = \frac{V}{R + j\omega L}$$

$$\therefore \boxed{i = \frac{V}{R + j\omega L}} \text{ at any instant}$$

$$\Rightarrow i = \frac{V}{R^2 + \omega^2 L^2} (R - j\omega L)$$

$$\Rightarrow \boxed{i = \frac{V(R - j\omega L)}{R^2 + \omega^2 L^2}}$$

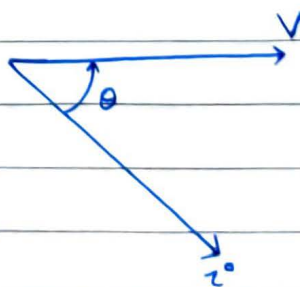$\therefore$  we get a phasor diagram like







$$\theta = \tan^{-1} \left( \frac{-\omega L}{R} \right)$$




## \* → SECOND ORDER CIRCUITS →

- First order circuits are characterised by first order diff. eq<sup>n</sup> and similarly second order diff. eq<sup>n</sup> represents second order circuits.
- First order circuits have one energy storage element (<sup>one</sup> capacitor or <sup>one</sup> inductor) but second order circuits have 2 storage elements.

eg -

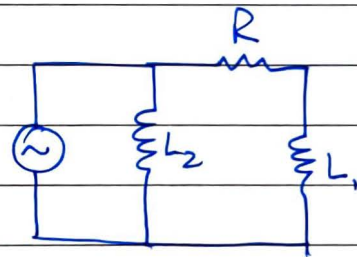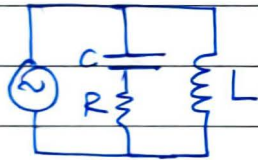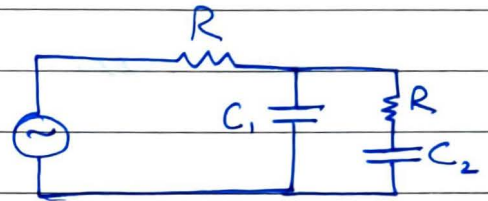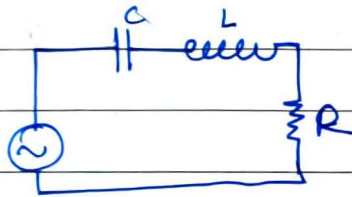

## → SOURCE FREE LCR circuits →

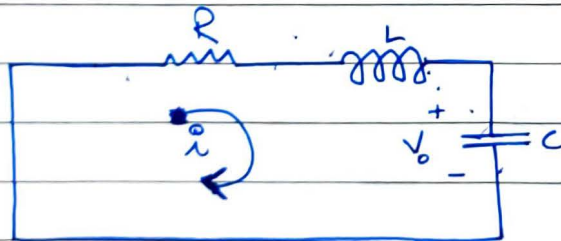

Let  $i(0) = i_0$   
And we can write

$$V_0 = \frac{1}{C} \int i dt$$

∴ writing KVL now

$$\frac{1}{C} \int i dt + L \frac{di}{dt} + iR = 0$$

Differentiating & dividing by L

$$\frac{i}{LC} + \frac{d^2 i}{dt^2} + \frac{R di}{L dt} = 0$$

$$\therefore \boxed{\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0} \quad - (i)$$

• we have an initial condition of form

$$Ri(0) + L \frac{di(0)}{dt} + V_0(0) = 0$$

$$\Rightarrow \boxed{\frac{di(0)}{dt} = -\frac{1}{L} (Ri_0 + V_0(0))}$$

• Now to solve - (i) we take an assumption (like 'Ansatz' in Physics)

$$\text{Let } i(t) = Ae^{st}$$

∴ Substituting in - (i)

$$Ae^{st} \left( s^2 + \frac{R}{L} s + \frac{1}{LC} \right) = 0$$

$$\Rightarrow s^2 + \frac{R}{L} s + \frac{1}{LC} = 0$$

$$\Rightarrow s = \frac{-R/L \pm \sqrt{\frac{R^2}{L^2} - \frac{4}{LC}}}{2}$$



$$\Rightarrow s = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\therefore s_1 = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$s_2 = \frac{-R}{2L} - \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$\therefore$  we have two solutions of  $i$  i.e.

$$i_1 = A_1 e^{s_1 t} \quad ; \quad i_2 = A_2 e^{s_2 t}$$

$\therefore$  we have a combined solution for  $i$  as

$$i = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

• we write

$$\left. \begin{aligned} s_1 &= -\alpha + \sqrt{\alpha^2 - \omega_0^2} \\ s_2 &= -\alpha - \sqrt{\alpha^2 - \omega_0^2} \end{aligned} \right\} \text{ where } \alpha = R/2L = \text{damping factor}$$


$$\omega_0 = \frac{1}{\sqrt{LC}} = \text{undamped natural frequency}$$

• Analysing values of  $\alpha$  and  $\omega_0$ , we could have 3 types of solutions of eq<sup>n</sup> (i)

& PTO

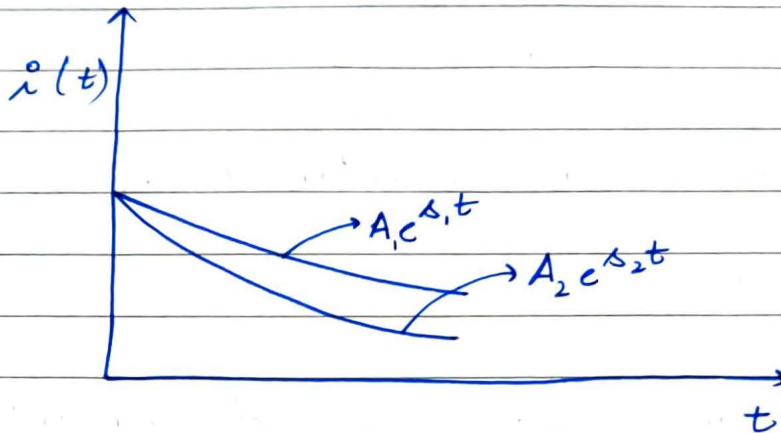1.  $\alpha > \omega_0$  i.e.  $\frac{R}{2L} > \frac{1}{\sqrt{LC}}$  (OVERDAMPED SYSTEM)

$$i(t) = A_1 e^{\Delta_1 t} + A_2 e^{\Delta_2 t}$$



{ Similar to overdamping in Physics }

2.  $\alpha = \omega_0$  i.e.  $\Delta_1 = \Delta_2 = -\alpha$  (CRITICAL DAMPING)

• we could write

$$i = A_1 e^{-\alpha t} + A_2 e^{-\alpha t} = A_3 e^{-\alpha t}$$

But note carefully that any second order eq<sup>n</sup> has 2 initial conditions! (Here there would be some  $i(0) = \text{const.}$  and  $(\frac{di}{dt})|_{(t=0)} = \text{const.}$ )

But from above eq<sup>n</sup>, we can see that we can get only one initial condition.  $\therefore$  this solution is somehow invalid.

•  $\therefore$  To find the correct solution, we follow the following procedure

$$\frac{d^2 i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{1}{LC} i = 0$$

$$\Rightarrow \frac{d}{dt} \underbrace{\left\{ \frac{di}{dt} + \kappa i \right\}}_f + \kappa \underbrace{\left\{ \frac{di}{dt} + \kappa i \right\}}_f = 0 \quad (\because \kappa^2 = \omega_0^2)$$

$$\Rightarrow \frac{df}{dt} + \kappa f = 0$$

$$\Rightarrow f = A_1 e^{-\kappa t}$$

$$\Rightarrow \frac{di}{dt} + \kappa i = A_1 e^{-\kappa t}$$

$$\Rightarrow A_1 = e^{\kappa t} \frac{di}{dt} + e^{\kappa t} \kappa i$$

$$\Rightarrow A_1 = \frac{d}{dt} (i e^{\kappa t})$$

$$\Rightarrow A_1 = \frac{d}{dt} (i e^{\kappa t})$$

$$\Rightarrow \int d(i e^{\kappa t}) = \int A_1 dt$$

$$\Rightarrow i e^{\kappa t} = A_1 t + A_2$$

$$\Rightarrow i = (A_1 t + A_2) e^{-\kappa t}$$



3.  $\alpha < \omega_0$  i.e.  $\frac{R}{2L} < \frac{1}{\sqrt{LC}}$  (UNDER DAMPED SYSTEM)

we can see

$$\cancel{s_1} \quad s_1 = -\alpha + \sqrt{-(\omega_0^2 - \alpha^2)}$$

$$\therefore \cancel{s_1} \quad s_1 = -\alpha + j\omega_d$$

$$s_2 = -\alpha - \sqrt{-(\omega_0^2 - \alpha^2)}$$

$$\therefore s_2 = -\alpha - j\omega_d$$

$$i = A_1 e^{-\alpha + j\omega_d} + A_2 e^{-\alpha - j\omega_d}$$

$$\Rightarrow i = [A_1 (\cos \omega_d + j \sin \omega_d) + A_2 (\cos \omega_d - j \sin \omega_d)] e^{-\alpha}$$

$$\Rightarrow i = [(A_1 + A_2) \cos \omega_d + j(A_1 - A_2) \sin \omega_d] e^{-\alpha}$$

$$\Rightarrow \boxed{i = [B_1 \cos \omega_d + j B_2 \sin \omega_d] e^{-\alpha}}$$

where  $B_1 = A_1 + A_2$  ;  $B_2 = A_1 - A_2$