

# भारतीय प्रौद्योगिकी संस्थान पटना

## Indian Institute of Technology Patna

Navin Government Polytechnic Campus, Patliputra Colony, Patna 800 013

### Basic Electrical Science-EE-101 Time: 3 hour, FM=50

Q-1 answers all parts of the questions.

5

- (a) Represent  $(123.4)_8$  into decimal number and binary number equivalent.  
(b) Find the value of  $(1000001-0110111)$  and  $(1111101+0110111)$   
(c) Convert  $(0.513)_{10}$  into octal. (d) Get the result in digital form  $(-15+7)$  and  $(-19-17)$  (e) Define gray codes and its importance.

Q-2 (a) Show maxterms and minterms for three binary variables by a table and verify by an example that it follows DeMorgans theorems.

2

(b) Simplify the following Boolean expressions to a minimum number of literals

2

(i)  $ABC + A'B + ABC'AC$

(ii)  $(x+y+z) + (x' + z')$

(c) converts each of the following functions into sum of product and product of sum form

2

(i)  $(AB+C)(B+C'D)$

(ii)  $x' + x(x+y')(y+z)$

Q-3 Solve the following Boolean functions using Karnaugh maps.

4

(i)  $F(A,B,C,D) = \Sigma(4,5,6,7,15)$

(ii)  $F(A,B,C,D) = \Sigma(2,3,6,10,12,13,14,15);$

(iii)  $ABC + A'B'C + AB'C' + A'BC$

(iv)  $AB'C + B'C'D' + BCD + ACD + A'B'C + A'BC'D$

Q-4 Write characteristic table of JK and D flip flops and design asynchronous up counter and synchronous down counter using any 3 flip flops.

5

Q-5 A speaker of  $9 \Omega$  is connected to  $10 \text{ V}$  source via an ideal transformer. The internal resistance of source is  $1 \Omega$ . Determine the turns ratio of transformer for which the speaker receives maximum power.

2

Q-6 A  $5 \text{ kVA}$ ,  $200/20 \text{ V}$  (rms) single phase transformer connected to a  $200 \text{ V}$  (rms) single phase supply draws a current of  $1 \angle 45^\circ \text{ A}$  (rms). Determine the load impedance  $Z_2$  connected to the secondary of the transformer. Assume ideal transformer.

2

Q-7 A single phase  $100 \text{ kVA}$ ,  $1000/100 \text{ V}$  transformer gave the following test results:

6

Open-circuit test (HV side open)

$100 \text{ V}$ ,  $6.0 \text{ A}$ ,  $400 \text{ W}$

Short-circuit test (LV side shorted)


$50 \text{ V}$ ,  $100 \text{ A}$ ,  $1800 \text{ W}$

Derive an approximate equivalent circuit referred to HV side.


Q-8 for the given instrumentation amplifier, using two ideal OP-AMPs, verify the following equation.

6


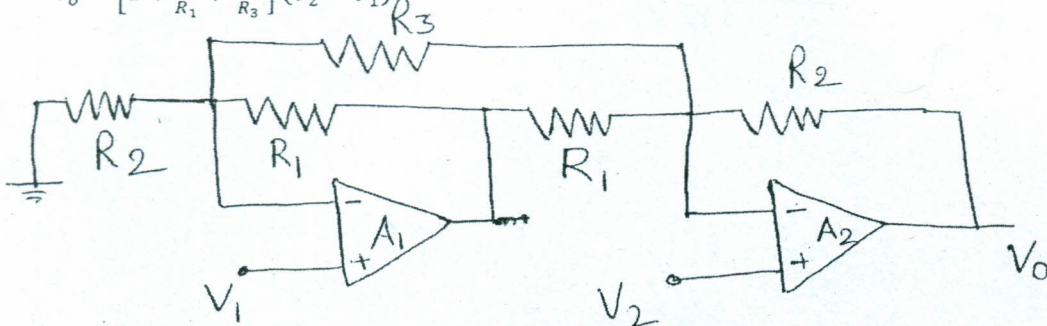
$$v_o = \left[ 1 + \frac{R_2}{R_1} + \frac{2R_2}{R_3} \right] (v_2 - v_1)$$



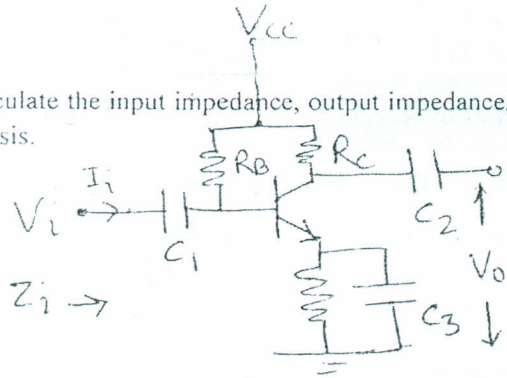
Q.-9 Calculate the input impedance, output impedance, voltage gain and current gain for the given circuit in case of BJT AC analysis. 6



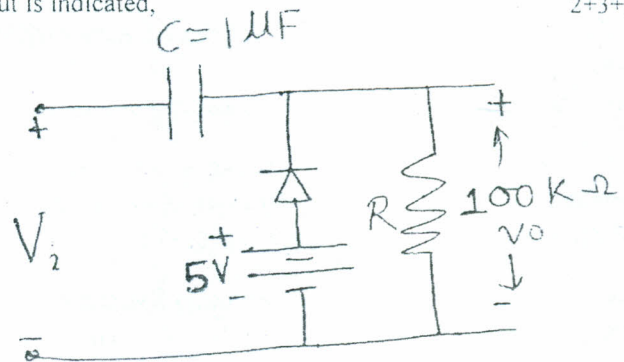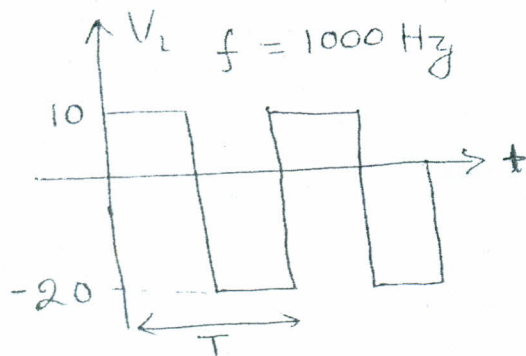Q.-10(a) Draw the  $v_o$  for the given network where input is indicated, 2+3+3



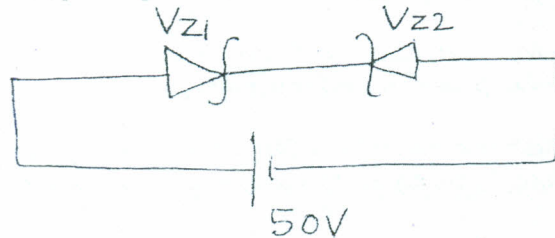(b) The Zener diode  $V_{Z1}$  given in figure has saturation current of 20 micro ampere and reverse breakdown voltage of 100V where as the corresponding values for diode  $V_{Z2}$  are 40 micro ampere and 40V. Determine the current through the circuit.



(c) The BJT in the given circuit has maximum  $I_{co}=2$  micro ampere and current amplification factor  $\beta_{min}=50$ , and  $\beta_{max}=150$ . Obtain the value of resistor that can prevent collector voltage falling below 8V.

