

Indian Institute of Technology Patna
Mid-Semester Examination, Autumn Semester 2011-2012
Electrical Sciences (EE101)

Full Marks: 40


Time: 2 hours

Answer All Questions

1. In the given circuit, the variable resistor (R_0) is adjusted until it dissipates maximum power from the circuit.

- Find the value of R_0 when it dissipates maximum power.
- Find the corresponding value of power dissipated through R_0 .
- Find the corresponding value of the percentage of total power dissipated through R_0 .


[5+1+1 = 7]

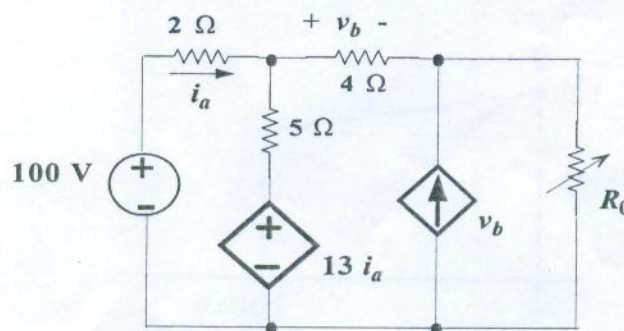

2. The switch in the given circuit is closed at $t = 0$ after being open for a long time.


- Find $i_1(0^-)$ and $i_2(0^-)$.
- Find $i_1(0^+)$ and $i_2(0^+)$.
- Find $i_1(t)$ for $t \geq 0$.
- Find $i_2(t)$ for $t \geq 0$.

[1+1+2+2 = 6]

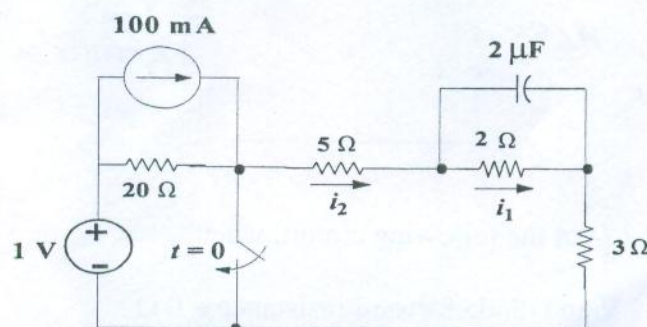

3. Find Thevenin equivalent circuit with respect to the terminals a, b of the circuit shown in the following figure.

[6]

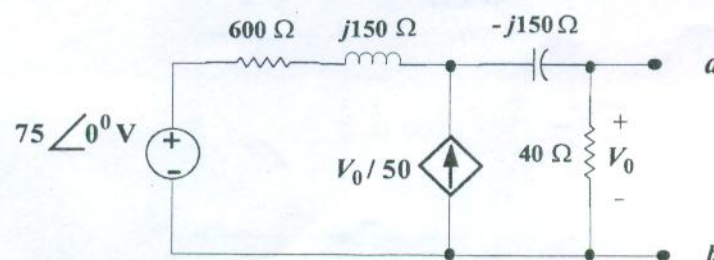


4. Define quiescent point in reference to ac-analysis of diode. Derive expression for diode small-signal resistance, which shows that diode small-signal resistance depends on quiescent point. [2+4 = 6]

5. For a Half-wave rectifier circuit, when a sinusoidal input is applied at the primary winding of transformer, derive expressions for (i) rms value of load current, (ii) Percentage voltage regulation (iii) Ripple factor of load current. [2+2+2 = 6]


6. (a) In a series RLC circuit $R = 2k\Omega$, $L = 1/40$ H and $C = 1/400$ μ F. Find the resonant frequency.

(b) A function is given by: $f(t) = \sin^2 t + \cos 2t$. Find the frequency components of $f(t)$.

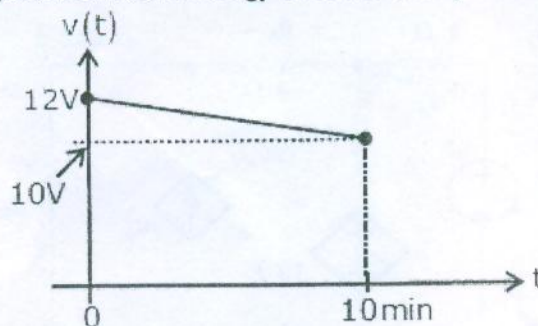(c) A fully charged mobile phone with a 12V battery is good for a 10minute talktime. Assume that, during the talk-time, the battery delivers a constant current of 2A and its voltage drops linearly from 12 V to 10V as shown in the figure. How much energy does the battery deliver during this talk-time?



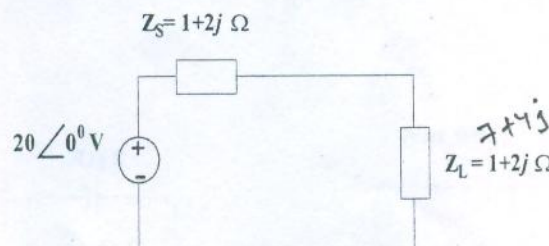(d) An AC source with peak voltage 20V and internal impedance $Z_s = 1 + 2j \Omega$ feeds a load of impedance $Z_L = 7 + 4j \Omega$ in the figure below. Find the real power, reactive power supplied to the load. Also find the power factor for the load.



- (e) Find the diode current I_D in the following circuit, when
- Diode is ideal
 - Cut-in voltage = 0.7 V and diode forward resistance = 0Ω
 - Cut-in voltage = 0.7 V and diode forward resistance = 30Ω

[1+1+2+2+3 = 9]

