

Indian Institute of Technology Patna
Mid-Semester Examination
Electrical Sciences (EE101)

2009 - 2010

Full Marks: 40

Time: 2 Hours

Answer all questions

1. Find the Thevenin equivalent at terminals $a-b$ in the circuit of Figure 1.

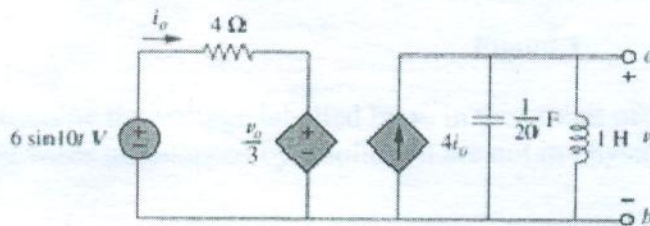


Figure 1

(7)

2. (a) Derive the expressions for natural response for a series RLC circuit for different possible values of R , L and C .
 (b) The switch in the circuit of Fig. 2 is moved from position a to b at $t = 0$. Determine $i(t)$ for $t > 0$.

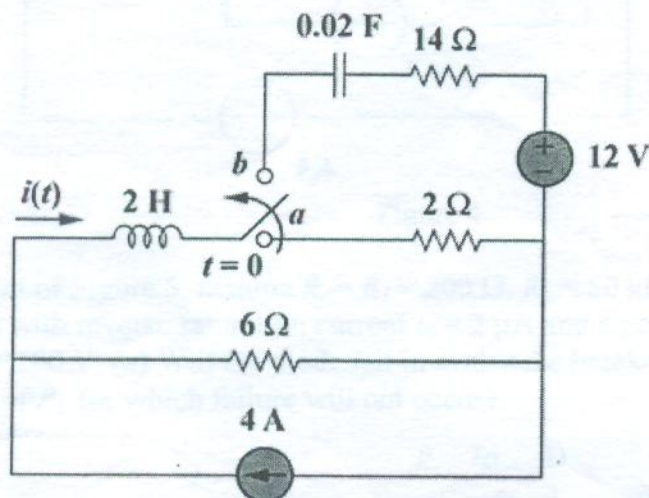


Figure 2

(3+5=8)

3. Find the frequency at which the phase shift between the input and output signals in a Wien Bridge network (given in Figure 3) is zero. Here, V_i and V_o represent phasors for input and output sinusoids. Find the corresponding gain $A_v = \frac{V_o}{V_i}$.

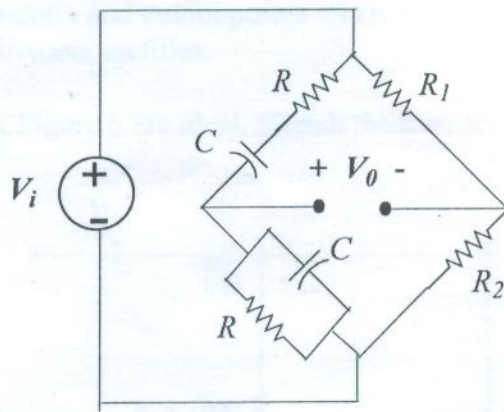


Figure 3

(5)

4. Determine the voltage labelled by v_a in the circuit of Figure 4 using supernode concept. Crossed wires not marked by a solid dot are not in physical contact.

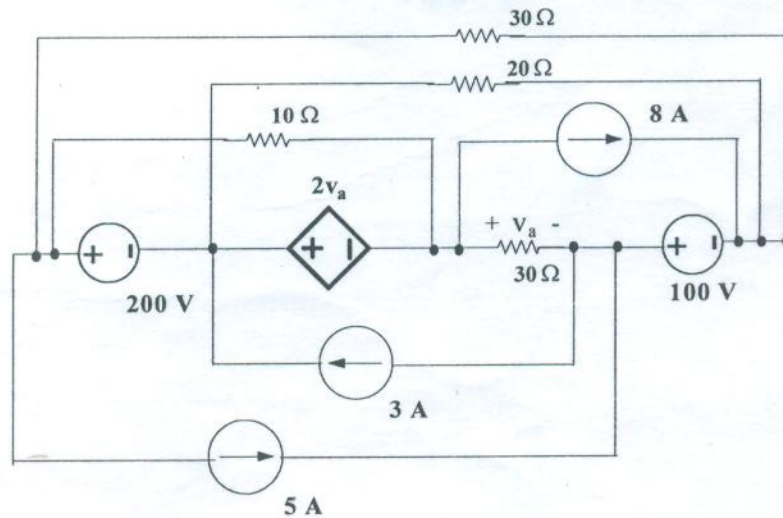


Figure 4

(5)

5. In the circuit of Figure 5, assume $R_s = R_I = 200 \Omega$, $R_L = 50 \text{ k}\Omega$ and $v_s = 400 \sin \omega t \text{ V}$. The diode is ideal with reverse saturation current $I_0 = 2 \mu\text{A}$ and a peak inverse voltage (PIV) rating of $V_R = 100 \text{ V}$. (a) Will the diode fail in avalanche breakdown? (b) If diode will fail, is there a value of R_L for which failure will not occur?

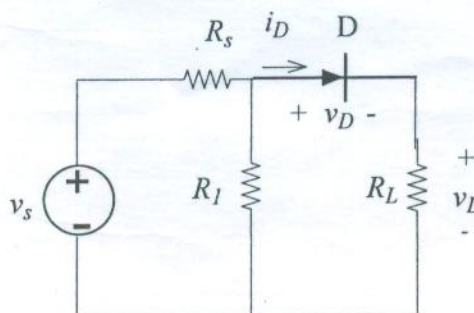


Figure 5

(5)

6. Derive the expressions for cutin and cutout points when a capacitor is connected in parallel with the load of a half-wave rectifier. (5)

7. The diodes in the circuit of Figure 6 are ideal. Sketch the transfer characteristic for $-20 \text{ V} \leq V_1 \leq 20 \text{ V}$.

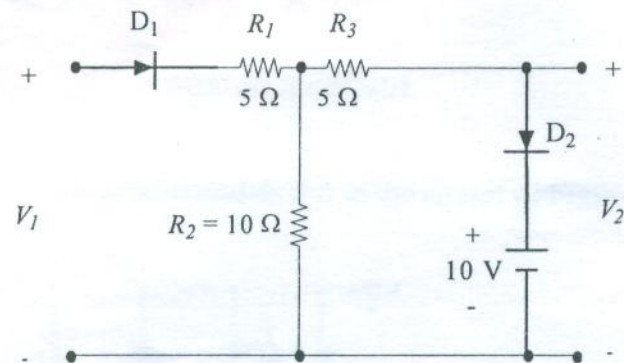


Figure 6 (5)