

Indian Institute of Technology Patna



End Semester Exam. (Autumn 2016)

Electrical Sciences (EE101)

Time: 3 Hrs

MM: 50

There are 8 questions in this paper. Answer all parts of a question at one place.
Figures in the right hand margin indicate marks. In case of a missing parameter value assume a suitable one.

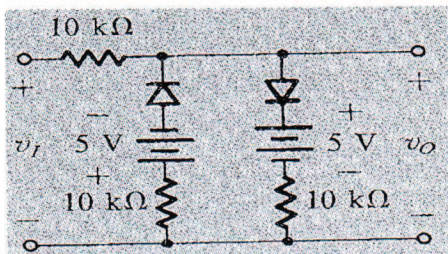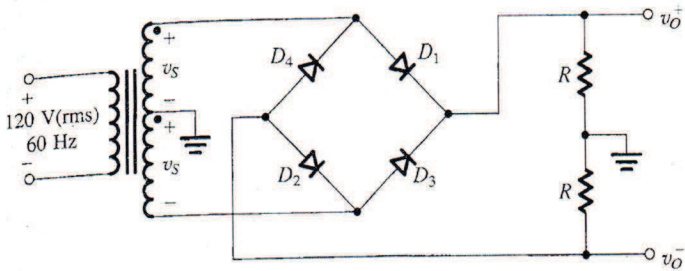Q No.	Questions	Marks
1.	(a) A cylindrically shaped section of n-type Si has a 1mm length and 0.1 mm^2 cross-sectional area. Calculate its conductivity and resistance (a) when it is purely intrinsic material, and (b) when it has a free electron density of $8 \times 10^{13} / \text{cm}^3$. (b) Compare the I-V plots of Si and Ge made diodes.	3 2
2.	(a) Explain the origin of the barrier voltage at a p-n junction. Discuss the effect of barrier voltage on drift and diffusion currents. (b) By how much does the built in voltage change if either side of impurity doping concentration is increased by a factor of 10. (c) Why built in voltage of a p-n junction diode can't be measured by a voltmeter?	2 1.5 1.5
3.	(a) Assuming the diodes to be ideal, describe the transfer characteristics of the circuit shown below 	3
	(b) Draw the circuits for positive and negative voltage doublers. Explain the working.	2
4.	(a) Sketch and clearly label the waveforms of v_o^+ and v_o^- . Consider $V_s = 5 \sin 120\pi t$. 	3
	(b) A 9.1 V Zener diode exhibits its nominal voltage at a test current of 28mA. At this current the incremental resistance is specified as 5Ω . Find V_{z0} of the zener model. Find the Zener voltage at a current of 10mA and at 100mA.	2

5. (a) With the help of a neat diagram explain the transistor action of npn BJT. 3
 (b) Draw and explain the input and output characteristics of CE configuration of BJT. 2
 (c) What is early effect? 1
6. (a) What is the transistor biasing? 2
 (b) The pnp transistor of the circuit given below (Fig 6.1) has $\beta=50$. Find the value of R_C to obtain $V_C = 5V$. What happens if the transistor is replaced with another with $\beta=100$. 2

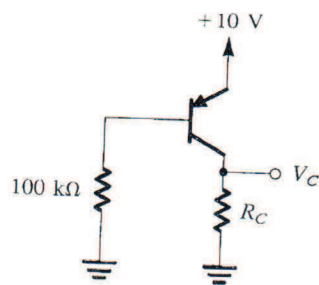


Fig 6.1


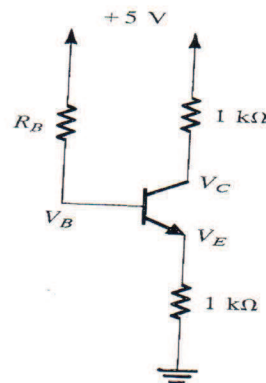


Fig 6.2

- (c) For the circuit of Fig 6.2, find V_B , V_C and V_E for $R_B = 10k\Omega$ and $\beta=100$. 2

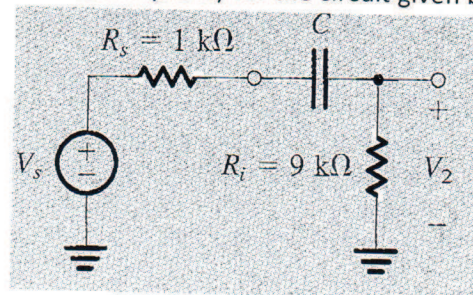7. (a) Draw a neat circuit of Instrumentation amplifier and also explain the working principle? 3
 Design an instrumentation amplifier for differential voltage gain of 20.
 (b) Using Ideal Op-amps, implement the input output relationship $V_o = 4V_1 + 3V_2 + 5V_3$. 2
 (c) What is the slew rate? Determine the maximum peak output voltage obtainable from an Op-amp circuit with a 100 kHz signal frequency. Slew rate is $0.5V/\mu s$. 2
8. (a) Derive the expression for 3-dB frequency in a first-order low pass filter circuit. 2
 (b) Draw the gain and phase responses for a first-order high pass filter circuit. 2
 (c) Find the transfer function and 3-dB frequency for the circuit given below. 3



- (d) Using operational amplifier, design a current amplifier with a current gain of 10. 2
 (e) Design an analog circuit which has two inputs (V_1 and V_2) and one output (V_o) with input-out relationship $V_o = V_2/V_1$. 2