



# भारतीय प्रौद्योगिकी संस्थान पटना Indian Institute of Technology Patna

Time: 3 Hours

Marks: 100

Subject: EE101 Electrical Science

Answer all questions.

Q.1 Given the Boolean function  $F = xy'z + x'y'z + w'xy + wx'y + wxy$

(a) Obtain the truth table of the function

(b) Draw the logic diagram using the original Boolean expression

(c) Simplify the function to a minimum number of literals using Boolean Algebra. [5]

Q.2 With the use of maps, find the simplest form in SUM of Products of the function  $F = fg$ , where  $f$  and  $g$  are respectively  $f = wxy' + y'z + w'yz' + x'yz'$  and  $g = (w+x+y+z')(x'+y'+z)(w'+y+z')$  [10]

Q.3 In a certain application, four inputs A, B, C, D (both true and complements forms are available) are fed to a logic circuit, producing an output F which operates a relay. The relay turns ON when  $F(A, B, C, D) = 1$  for the following states of the inputs (A B C D): 0000, 0010, 0101, 0110, 1101 and 1110. States 1000 and 1001 do not occur, and for the remaining states, the relay is OFF. Minimize F with the help of K-Map and realize it using a minimum number of 3 input NAND gates. [7]

Q.4 The circuit diagram of a synchronous counter is shown in Fig. 1. Determine the sequence of states of the counter assuming that initial state is 000. Give your answer in a tabular form showing the present states ( $Q_{A(n)}, Q_{B(n)}, Q_{C(n)}$ ), JK inputs ( $J_A, K_A, J_B, K_B, J_C, K_C$ ), and the next state ( $Q_{A(n+1)}, Q_{B(n+1)}, Q_{C(n+1)}$ ). Find the table, determine the modulus of the counter. [8]

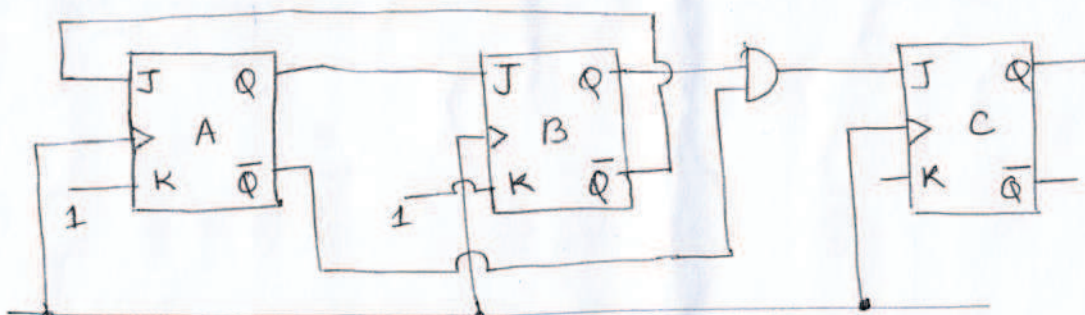


Figure 1

Q.5 (a) Represent the decimal number into binary equivalent. -27, -211, 27, 211.

(b) Write short note on not more than 2 sentences. (i) Linearity Principle, (ii) Decoder, (iii) Priority Encoder, (iv) Thevenin Theorem & (v) Norton Theorem. [10]

Q.6 (a) Use Nodal Analysis to determine the node voltage in Fig. 2.

(b) Find the Nodal voltages of the circuits in Fig. 3. [10]

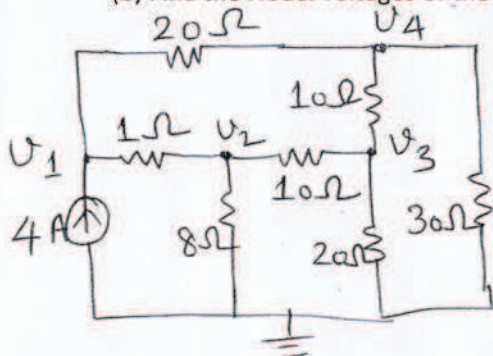


Figure: 2

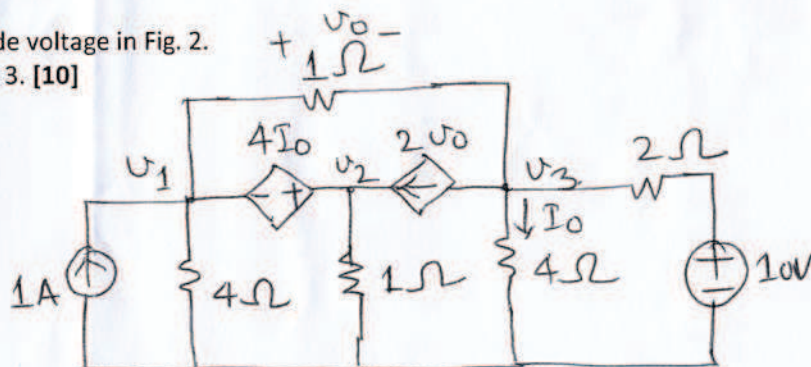


Figure: 3



Q.7 Determine the Gain  $v_o/v_i$  of the circuit in Fig. 4. [5]

Q.8 Calculate  $I_o$  in the circuit in Fig. 5. [5]

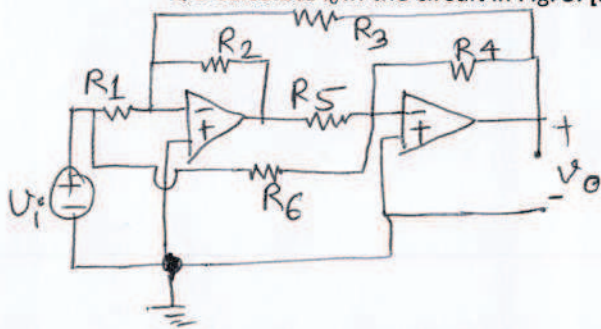


Figure: 4

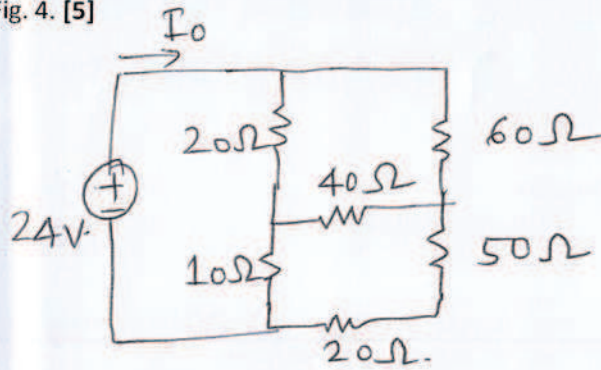


Figure: 5

Q.9 For the circuit in Fig. 6, use Superposition to find  $i$ . Calculate the power delivered to 3 Ohm. [10]

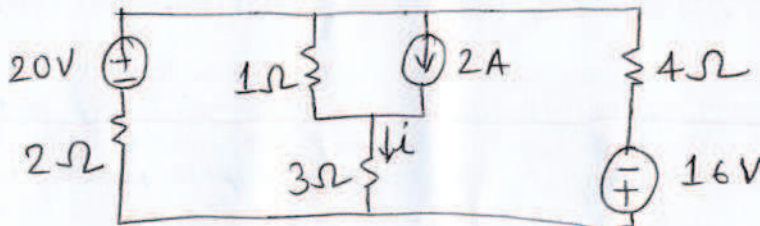


Figure: 6

Q.10 (a) Obtain Thevenin and Norton equivalent circuits at terminal a-b of the circuit in fig. 7. Calculate maximum power delivered to the load. [10]

(b) Find the Thevenin equivalent of the circuit in Fig. 8. Calculate maximum power delivered to the load. [10]

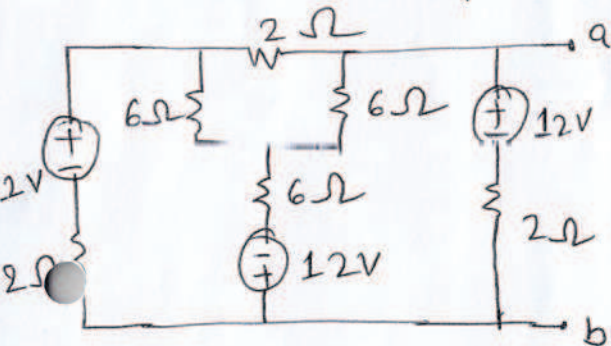


Figure: 7

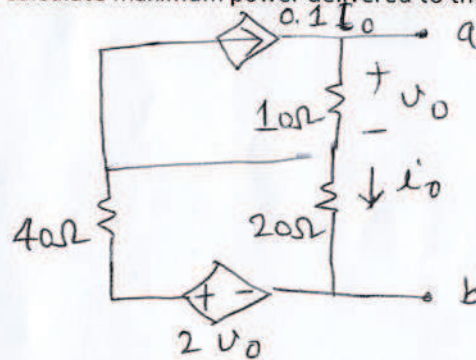


Figure: 8

Q.11 In the circuit shown in Fig. 9, Find  $i_o$ ,  $v_o$ , and  $I$  for all time, assuming that the switch was open for a long time. [10]

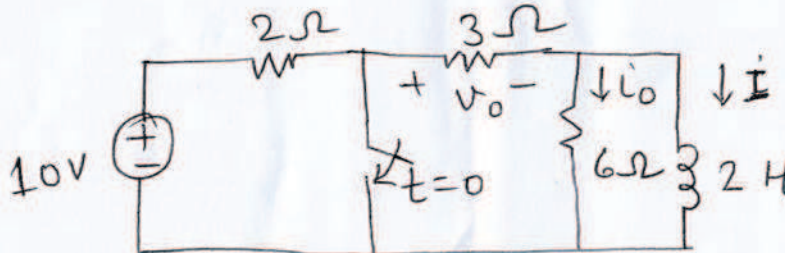


Figure: 10