

Indian Institute of Technology Patna
Mid-Semester Examination, Autumn Semester 2010-2011
Electrical Sciences (EE101)

Full Marks: 40

Time: 2 hours

Answer All Questions

1. Find the expressions for complete response, natural response, forced response, transient response and steady-state response for a RL circuit when a step input is applied to the circuit. [7]
2. Calculate the power dissipated in each circuit element in the network of Fig. 1.

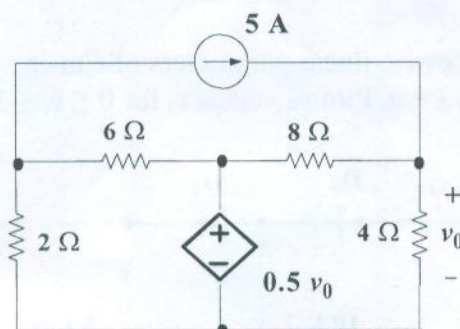


Fig. 1

[4]

3. Use the superposition principle to find i_0 and v_0 in the circuit of Fig. 2.

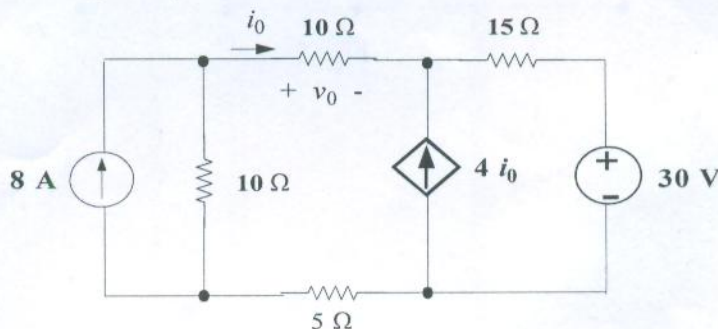


Fig. 2

[6]

4. In Fig. 3 the switch has been maintained in open state for a long time and it is closed at $t = 0$. Find $i(t)$ for $t > 0$.

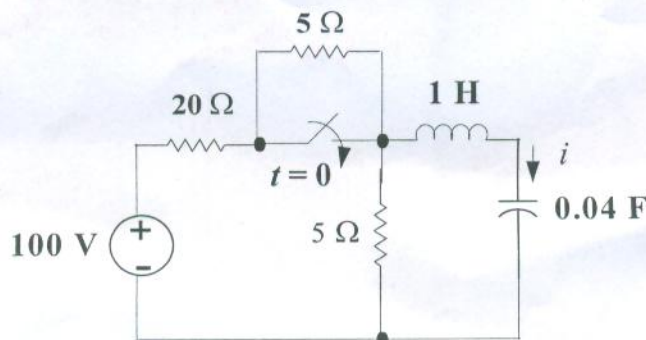


Fig. 3

[7]

5. Obtain Thevenin and Norton equivalent circuits for the network shown in Fig. 4 in reference to terminals $a-b$.

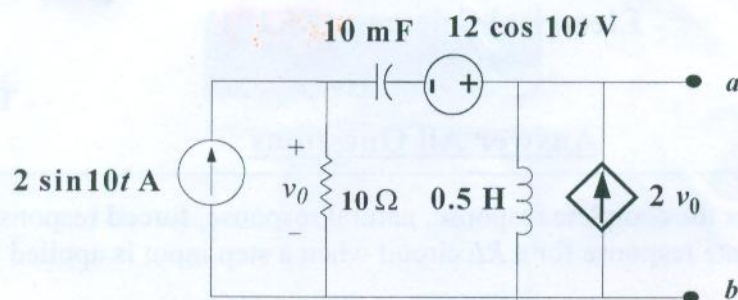


Fig. 4

[8]

6. Each diode in Fig. 5 has piecewise linear parameters of Cut-in voltage (i.e., V_γ) = 0 and Forward diode resistance (i.e., r_f) = 0. Plot v_o versus v_i for $0 \leq v_i \leq 30$ V.

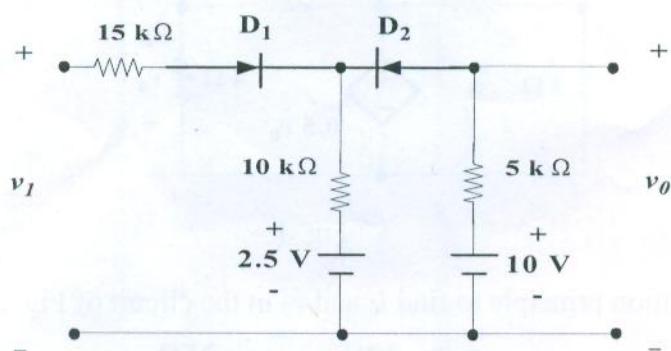


Fig. 5

[8]