


Indian Institute of Technology Patna  
Department of Electrical Engineering

EE101 - Electrical Sciences  
Autumn - 2015  
End Sem Exam  
21 November 2015


There are 5 problems. They carry equal marks.

$$(5 \times 10 = 50)$$

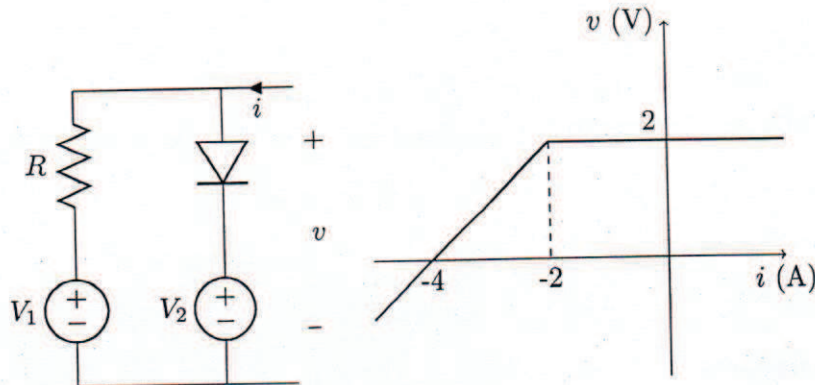
1. (a) Consider the circuit and its  $v-i$  characteristics. Find  $V_1$ ,  $V_2$  and  $R$ .



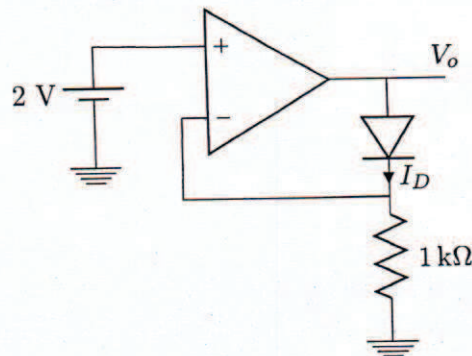- (b) Consider the circuit. Find  $V_o$  and  $I_D$ . Use 0.7 V model for diode.




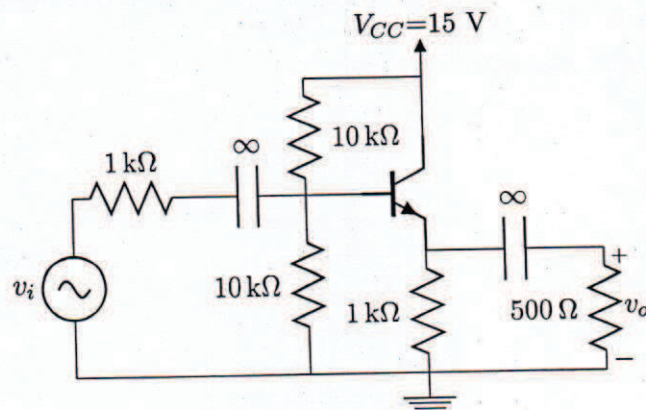2. Consider the circuit. Assume  $\beta = 100$  and  $V_{BE} = 0.7$  V.



- Determine the operating point.
- Draw the small signal model.
- Find the small signal voltage gain.
- Find the input and output resistance from the small signal model.

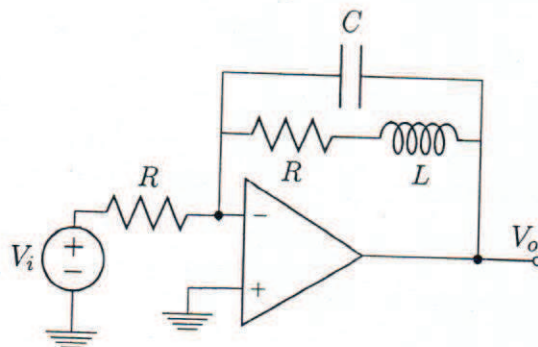3. Consider the op-amp circuit. Assume that the op-amp is ideal.




- (a) Find the differential equation that relates  $V_o$  to  $V_i$ .  
 (b) Let  $V_i = V_m \cos(\omega t)$ . Find the sinusoidal steady state output  $V_o$  that has the following form.

$$V_o = A \cos(\omega t + \phi)$$

4. Consider the circuit. The terminal characteristics of nonlinear element is

$$i_N = ae^{bv_N}$$

where  $a$  and  $b$  are constants.

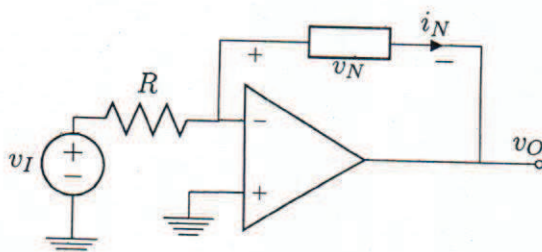

- (a) Find the expression that relates  $v_O$  to  $v_I$ .  
 (b) if  $v_I$  consists of DC and small signal ( $V_I + v_i$ ), the output can also be represented as  $v_O = V_O + v_o$ . Draw the small signal model.  
 (c) Find the small signal gain expression  $\frac{v_o}{v_i}$ .  
 5. (a) Design a three input digital circuit that should give a high output whenever two adjacent bits are high. Implement the circuit using only NAND gates.  
 (b) Given the truth table for the logic function F:

A	B	C	F
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	1

- i. Write the Product of Sums (POS) expression.  
 ii. Find the minimum POS expression.  
 iii. Implement the minimum POS using only NOR gates.