

# CS225 Switching Theory

Dr. Somanath Tripathy

Associate Professor

Network Security Lab

Department of Computer Science and Engineering

Indian Institute of Technology Patna

# Previous Class

- Switching Algebra
  - Switching circuit
  - Propositional calculus

This Class

**Minimization/ Simplification of Switching Functions**

# Last class


Q1. Solve the following expression

$$(x + y'z')(y + x'z')(z + x'y')$$

Ans:

$$\begin{aligned} & (x + y'z')(y + x'z')(z + x'y') \\ = & (xy + xx'z' + y'z'y + y'z'x'z')(z + x'y') \\ = & (xy + 0 + 0 + x'y'z')(z + x'y') \\ = & xyz + xyx'y' + x'y'z'z + x'y'z'x'y' \\ = & xyz + 0 + 0 + x'y'z' \\ = & xyz + x'y'z' \end{aligned}$$

# Combinational Circuit

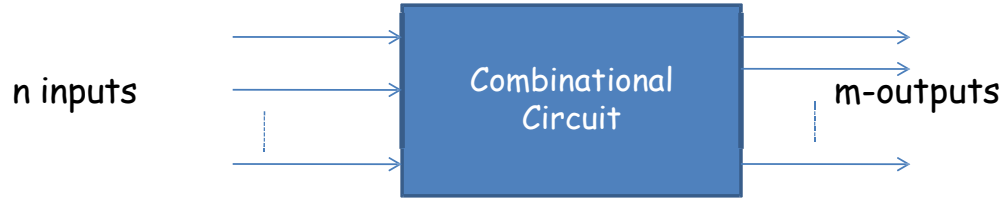


Design procedure:  
from the specification

1. Determine the required number of inputs and outputs
2. Derive the truth table
3. Find the Simplified Boolean expression for each output as a function of the input variable
4. Draw the logic diagram
5. Verify the correctness
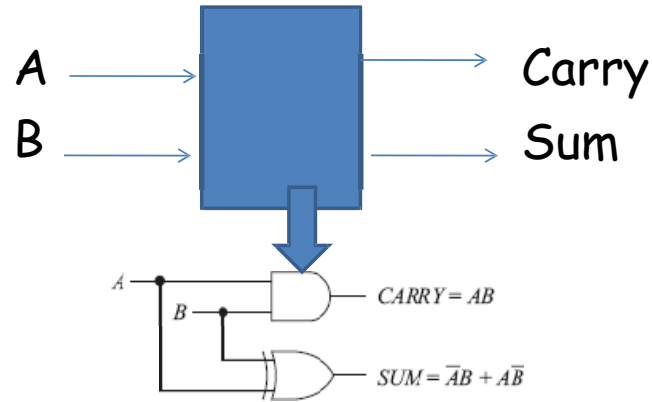
# EX.1: Binary Adder

- Half Adder:
- Four cases to remember ( Two single-bit addition)
  - $0+0=0$
  - $0+1=1$
  - $1+0=1$
  - $1+1=10$  (Carry has been generated)



# Combinational Circuit

- Analysis
  1. Find the Boolean functions for each gate and obtain the output
  2. Repeat step 1 until the output(s) of the circuit is obtained
  3. Obtain the output Boolean function in terms of input variables


Find the simplified Boolean expression!  
with minimum terms\ literals

# Definitions

- Literals  $x_i$  or  $x_i'$
- Product Term  $x_2 x_1' x_0$
- Sum Term  $x_2 + x_1' + x_0$
- Minterm of  $n$  variables: A product of  $n$  literals in which every variable appears **exactly** once.
- Maxterm of  $n$  variables: A sum of  $n$  literals in which every variable appears **exactly** once.
- Adjacency of minterms (maxterms): Two minterms (maxterms) are adjacent if they differ by only one variable.



# Implementation

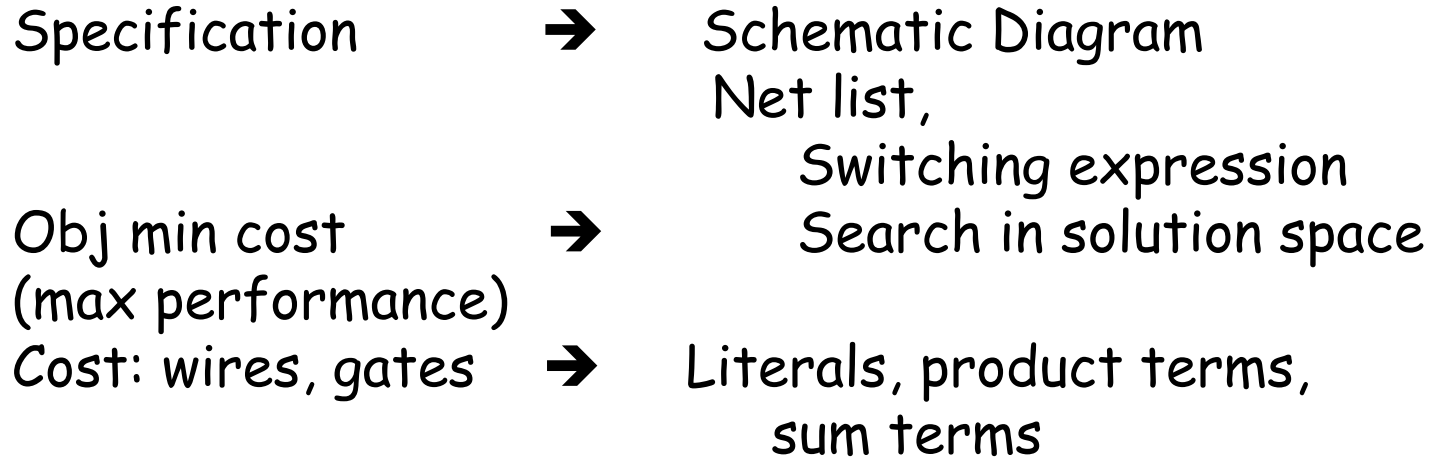

For two level logic (sum of products or product of sums),  
we want to minimize # of terms, and # of literals

# Simplifying Switching Functions

---

Finding an equivalent switching expression that minimizes some cost criteria:

1. Minimize literal count
2. Minimize literal count in sum-of-products (or product-of-sums) expression
3. Minimize number of terms in a sum-of-products expression provided no other expression exists with the same number of terms and fewer literals

$$\begin{aligned}\text{Example: } f(x,y,z) &= x'yz' + x'y'z + xy'z' + x'yz + xyz + xy'z \\ &= x'z' + y'z' + yz + xz\end{aligned}$$

# Implementation: Specification $\Rightarrow$ Logic Diagram

Karnaugh Map: A 2-dimensional truth table

Boolean expressions can be minimized by combining terms

K-maps minimize equations graphically

## Flow 1: Boolean Algebra

1. Specification
2. Truth table
3. Sum of products (SOP) or product of sums(POS) canonical form
4. Reduced expression using Boolean algebra
5. Schematic diagram of two level logic

## Flow 2: K Map

1. Specification
2. Truth Table
3. Karnaugh Map (truth table in two dimensional space)
4. Reduce using K-Maps
5. Reduced expression (SOP or POS)
6. Schematic diagram of two level logic

## K-Map: Truth Table in 2 Dimensions

### 2- Variables Truth Table      2- Variables K-Map

I D	A	B	f(A,B)
0	0	0	0
1	0	1	1
2	1	0	1
3	1	1	1

	B = 0	B = 1
A = 0	0	1
A = 1	1	1

Algebraic procedure to combine terms using the  $Aa + Aa' = A$  rule

$$f(A,B) = A + B$$

# The Map Method

Karnaugh map: modified form of truth table

$z \backslash xy$	00	01	11	10
0	0	2	6	4
1	1	3	7	5

(a) Location of minterms in a three variable map.

$z \backslash xy$	00	01	11	10
0		1	1	
1			1	

(b) Map for function  $f(x, y, z) = \sum(2, 6, 7) = yz' + xy$

$yz \backslash wx$	00	01	11	10
00	0	4	12	8
01	1	5	13	9
11	3	7	15	11
10	2	6	14	10

(c) Location of minterms in a four-variable map.

$yz \backslash wx$	00	01	11	10
00		1	1	1
01		1	1	
11			1	
10			1	

(d) Map for function  $f(w, x, y, z) = \sum(4, 5, 8, 12, 13, 14, 15) = wx + xy' + wy'z'$

# Simplification and Minimization of Functions

Cube: collection of  $2^m$  cells, each adjacent to  $m$  cells of the collection

- Cube is said to **cover** these cells
- Cube expressed by a product of  $n-m$  literals for a function containing  $n$  variables
- $m$  literals not in the product said to be **eliminated**

Example:  $w'xy'z' + w'xy'z + wxy'z' + wxy'z$

$$= xy'(w'z' + w'z + wz' + wz)$$
$$= xy'$$

yz \ wx	00	01	11	10
00		1	1	1
01		1	1	
11			1	
10			1	

(d) Map for function  $f(w, x, y, z) = \sum(4, 5, 8, 12, 13, 14, 15) =$

$$wx + xy' + wy'z'$$

# Minimization (Contd.)

Example:

Use of cell 6 in forming both cubes justified by idempotent law

z \ xy	00	01	11	10
0	0	2	6	4
1	1	3	7	5

(a) Location of minterms in a three-variable map.

z \ xy	00	01	11	10
0		1	1	
1			1	

(b) Map for function  
 $f(x, y, z) = \sum(2, 6, 7) = yz' + xy$

Corresponding algebraic manipulations:

$$\begin{aligned}f &= x'yz' + xyz' + xyz \\&= x'yz' + xyz' + xyz' + xyz \\&= yz'(x' + x) + xy(z' + z) \\&= yz' + xy\end{aligned}$$

Thanks