

Switching Theory Lab – CS226

Name: M. Maheeth Reddy Roll No.: 1801CS31

Date: 09-May-2020

Lab No.: 13

Ans 1:

Source Code:

```
// Binary to Gray Code Converter
module p1(gray,binary);
    // Mode Declaration
    input [3:0] binary;    // Binary Form
    output [3:0] gray;     // Gray Form

    assign gray[3] = binary[3];
    assign gray[2] = binary[3] ^ binary[2];
    assign gray[1] = binary[2] ^ binary[1];
    assign gray[0] = binary[1] ^ binary[0];
endmodule
```

Testbench:

```
module tb_p1();
    // Mode Declaration
    reg [3:0] num;
    wire [3:0] op;

    p1 UUT (op,num);    // Instantiate p1


    // Testcase: All 4-bit binary numbers
    initial begin
        num = 4'b0000;
        repeat(15) begin
            #10 num = num + 1;
        end
    end

    initial begin
        $display("binary    gray");
        $monitor(" %b      %b",num,op);
    end
endmodule
```

Text Output

```
VSIM 27> run
# binary    gray
# 0000      0000
# 0001      0001
# 0010      0011
# 0011      0010
# 0100      0110
# 0101      0111
# 0110      0101
# 0111      0100
# 1000      1100
# 1001      1101
# 1010      1111
# 1011      1110
# 1100      1010
# 1101      1011
# 1110      1001
# 1111      1000
```

Simulated Waveform

 

Simulation Time: 160ns

Ans 2:

Source Code:

// Module for given Sequential Circuit

```
module p2 (Y,S,clk);
    output Y;          // Output Y
    input S, clk;

    wire S1,S2;
    reg [2:1] S_prev;  // Stores previous values of S

    assign S2 = S_prev[2]; // Value of S before 2 clock cycles
    assign S1 = S_prev[1]; // Value of S before 1 clock cycle

    assign Y = (S & S1 & S2) | (~S & ~S1 & ~S2);

    always @ (posedge clk) begin
        S_prev = {S, S_prev[2]};
    end
endmodule
```

Testbench:

// Testbench for p2.v

```
module tb_p2();
    // Mode Declaration
    wire Y, S1, S2;
    reg S, clk;

    p2 UUT (Y, S, clk); //Instantiate p2

    always #9 clk = ~clk;

    // Assign S1 and S2
    assign S1 = UUT.S_prev[2];
    assign S2 = UUT.S_prev[1];

    initial begin
        clk = 0;
        UUT.S_prev = 2'b00;

        S = 1; #10;
        S = 0; #40;
        S = 1; #60;
```

Text Output

VSIM 37> run

# time=0	clk=0	S=1	S1=0	S2=0	Y=0
# time=9	clk=1	S=1	S1=1	S2=0	Y=0
# time=10	clk=1	S=0	S1=1	S2=0	Y=0
# time=18	clk=0	S=0	S1=1	S2=0	Y=0
# time=27	clk=1	S=0	S1=0	S2=1	Y=0
# time=36	clk=0	S=0	S1=0	S2=1	Y=0
# time=45	clk=1	S=0	S1=0	S2=0	Y=1
# time=50	clk=1	S=1	S1=0	S2=0	Y=0
# time=54	clk=0	S=1	S1=0	S2=0	Y=0
# time=63	clk=1	S=1	S1=1	S2=0	Y=0
# time=72	clk=0	S=1	S1=1	S2=0	Y=0
# time=81	clk=1	S=1	S1=1	S2=1	Y=1
# time=90	clk=0	S=1	S1=1	S2=1	Y=1
# time=99	clk=1	S=1	S1=1	S2=1	Y=1
# time=108	clk=0	S=1	S1=1	S2=1	Y=1
# time=110	clk=0	S=0	S1=1	S2=1	Y=0
# time=117	clk=1	S=0	S1=0	S2=1	Y=0
# time=126	clk=0	S=0	S1=0	S2=1	Y=0
# time=135	clk=1	S=0	S1=0	S2=0	Y=1
# time=144	clk=0	S=0	S1=0	S2=0	Y=1
# time=153	clk=1	S=0	S1=0	S2=0	Y=1
# time=162	clk=0	S=0	S1=0	S2=0	Y=1
# time=171	clk=1	S=0	S1=0	S2=0	Y=1
# time=180	clk=0	S=0	S1=0	S2=0	Y=1
# time=189	clk=1	S=0	S1=0	S2=0	Y=1
# time=190	clk=1	S=1	S1=0	S2=0	Y=0
# time=198	clk=0	S=1	S1=0	S2=0	Y=0
# time=207	clk=1	S=1	S1=1	S2=0	Y=0
# time=216	clk=0	S=1	S1=1	S2=0	Y=0
# time=225	clk=1	S=1	S1=1	S2=1	Y=1
# time=230	clk=1	S=0	S1=1	S2=1	Y=0
# time=234	clk=0	S=0	S1=1	S2=1	Y=0
# time=243	clk=1	S=0	S1=0	S2=1	Y=0
# time=250	clk=1	S=1	S1=0	S2=1	Y=0
# time=252	clk=0	S=1	S1=0	S2=1	Y=0
# time=261	clk=1	S=1	S1=1	S2=0	Y=0
# time=270	clk=0	S=0	S1=1	S2=0	Y=0
# time=279	clk=1	S=0	S1=0	S2=1	Y=0
# time=288	clk=0	S=0	S1=0	S2=1	Y=0
# time=297	clk=1	S=0	S1=0	S2=0	Y=1


```

S = 0; #80;
S = 1; #40;
S = 0; #20;
S = 1; #20;
S = 0; #20;
end

// Display all parameters
initial begin
    $monitor("time=%g clk=%b S=%b S1=%b S2=%b Y=%b", $time, clk, S, S1, S2, Y);
end
endmodule

```

Simulated Waveform

 

Simulation Time: 300ns
1 Clock Cycle: 9ns

Ans 3:

Source Code:

```
// Module for given 16-bit ALU
module p3(op, zero_flag, opmode, ip1, ip2);
    // Mode Declaration
    input [15:0] ip1,ip2;    // ALU Inputs
    input [2:0] opmode;      // ALU Operation Mode
    output reg [15:0] op;    // ALU Output
    output zero_flag;        // ALU Zero Flag

    always @(opmode or ip1 or ip2)
        case(opmode)
            3'b000: op = ip1 + ip2;
            3'b001: op = ip1 - ip2;
            3'b010: op = ip1 ^ ip2;
            3'b011: op = ip1 && ip2;
            3'b100: op = ip1 || ip2;
            3'b101: op = ip1 + 16'b0000_0001;
            3'b110: op = ip1 << 1;
            3'b111: op = ip1 >> 1;
            default: op = 3'bx;
        endcase

    assign zero_flag = (op == 16'b0);
endmodule
```

Test Bench:

```
// Testbench for p3.v
module tb_p3();
    // Mode Declaration
    reg [2:0] opmode;
    reg [15:0] ip1,ip2;
    wire zero_flag;
    wire [15:0] op;

    p3 UUT (op, zero_flag, opmode, ip1, ip2);    // Instantiate p3

    // For ip1 and ip2, obtain outputs for each mode
    initial begin
        ip1 = 16'b0010_0001; ip2 = 16'b1001_0001; opmode = 3'b000; #10;
        ip1 = 16'b1001_0001; ip2 = 16'b0010_0001; opmode = 3'b001; #10;
        ip1 = 16'b0101_0101; ip2 = 16'b1111_1111; opmode = 3'b010; #10;
        ip1 = 16'b0011_0011; ip2 = 16'b0101_0101; opmode = 3'b011; #10;
        ip1 = 16'b0011_0011; ip2 = 16'b0101_0101; opmode = 3'b100; #10;
        ip1 = 16'b0011_1111; ip2 = 16'bx;          opmode = 3'b101; #10;
    end
```

Text Output

```
VSIM 54> run
# opmode = 000
# ip1 = 0000000000100001
# ip2 = 0000000010010001
# op = 0000000010110010
# zero_flag = 0
# -----
# opmode = 001
# ip1 = 0000000010010001
# ip2 = 0000000000100001
# op = 0000000001110000
# zero_flag = 0
# -----
# opmode = 010
# ip1 = 0000000001010101
# ip2 = 0000000011111111
# op = 0000000010101010
# zero_flag = 0
# -----
# opmode = 011
# ip1 = 0000000000110011
# ip2 = 0000000001010101
# op = 0000000000000001
# zero_flag = 0
# -----
```

```

        ip1 = 16'b0011_1111; ip2 = 16'bx;          opmode = 3'b110; #10;
        ip1 = 16'b0011_1111; ip2 = 16'bx;          opmode = 3'b111;
        #10;
    end

    // Display all parameters
    initial begin
        $monitor("ip1=%b ip2=%b opmode=%b
                op=%b zero_flag=%b",
                ip1,ip2,opmode,op,zero_flag);
    end
endmodule

```


Text Output

```

# opmode = 100
# ip1 = 0000000000110011
# ip2 = 0000000001010101
# op  = 0000000000000001
# zero_flag = 0
# -----
# opmode = 101
# ip1 = 0000000000111111
# ip2 = xxxxxxxxxxxxxxxxxx
# op  = 0000000001000000
# zero_flag = 0
# -----
# opmode = 110
# ip1 = 0000000000111111
# ip2 = xxxxxxxxxxxxxxxxxx
# op  = 0000000001111110
# zero_flag = 0
# -----
# opmode = 111
# ip1 = 0000000000111111
# ip2 = xxxxxxxxxxxxxxxxxx
# op  = 0000000000011111
# zero_flag = 0
# -----

```


Simulation Waveform

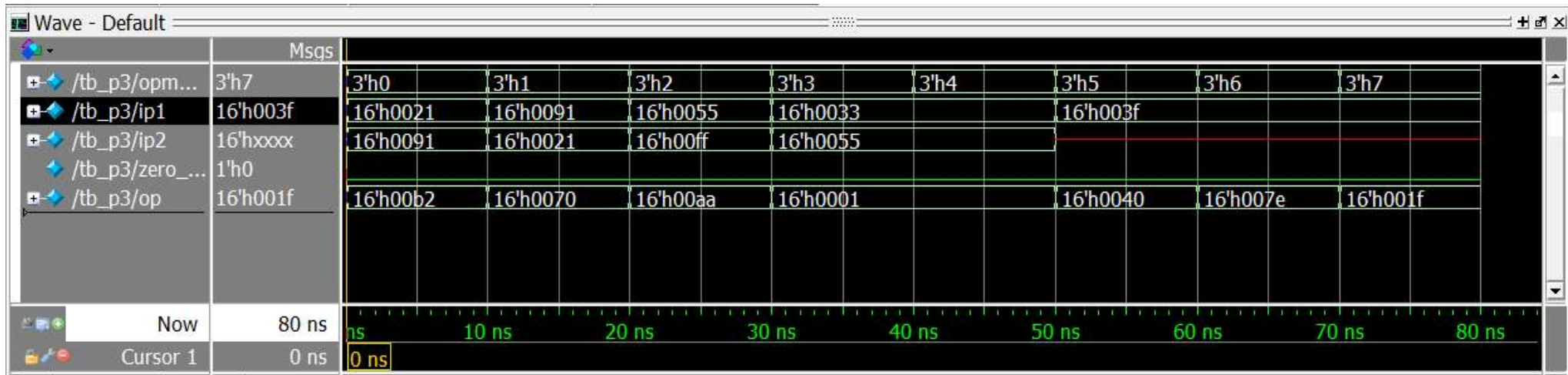

Simulation Time: 80ns

Ans 4:

Source Code:

```
// Module for Encoder
module p4(op,z1,z2,z3,z4,z5,z6,z7,z8);
    // Mode Declaration
    // Sensor Signal for each zone
    input z1,z2,z3,z4,z5,z6,z7,z8;

    // Output
    output [2:0] op;

    assign op[0] = (z2|z4|z6|z8);
    assign op[1] = (z3|z4|z7|z8);
    assign op[2] = (z5|z6|z7|z8);
endmodule
```

Test bench:

```
// Testbench for p4.v
module tb_p4();
    // Mode Declaration
    reg z1,z2,z3,z4,z5,z6,z7,z8;
    wire [2:0] op;

    // Instantiate p4
    p4 UUT (op,z1,z2,z3,z4,z5,z6,z7,z8);

    // Testcase: Only one zone is intruded one time
    initial begin
        {z1,z2,z3,z4,z5,z6,z7,z8} = 8'b10000000;
        #10;
        {z1,z2,z3,z4,z5,z6,z7,z8} = 8'b01000000;
        #10;
        {z1,z2,z3,z4,z5,z6,z7,z8} = 8'b00100000;
        #10;
        {z1,z2,z3,z4,z5,z6,z7,z8} = 8'b00010000;
        #10;
        {z1,z2,z3,z4,z5,z6,z7,z8} = 8'b00001000;
        #10;
        {z1,z2,z3,z4,z5,z6,z7,z8} = 8'b00000100;
        #10;
        {z1,z2,z3,z4,z5,z6,z7,z8} = 8'b00000010;
        #10;
        {z1,z2,z3,z4,z5,z6,z7,z8} = 8'b00000001;
        #10;
    end
```

Text Output

VSIM 58> run

#	z1=1	z2=0	z3=0	z4=0	z5=0	z6=0	z7=0	z8=0	op=000
#	z1=0	z2=1	z3=0	z4=0	z5=0	z6=0	z7=0	z8=0	op=001
#	z1=0	z2=0	z3=1	z4=0	z5=0	z6=0	z7=0	z8=0	op=010
#	z1=0	z2=0	z3=0	z4=1	z5=0	z6=0	z7=0	z8=0	op=011
#	z1=0	z2=0	z3=0	z4=0	z5=1	z6=0	z7=0	z8=0	op=100
#	z1=0	z2=0	z3=0	z4=0	z5=0	z6=1	z7=0	z8=0	op=101
#	z1=0	z2=0	z3=0	z4=0	z5=0	z6=0	z7=1	z8=0	op=110
#	z1=0	z2=0	z3=0	z4=0	z5=0	z6=0	z7=0	z8=1	op=111

 

```

end

// Display all parameters
initial begin
    $monitor("z1=%b z2=%b z3=%b z4=%b z5=%b z6=%b z7=%b z8=%b op=%b", z1, z2, z3, z4
, z5, z6, z7, z8, op);
end
endmodule

```

Simulation Waveform



Simulation Time: 80ns

Ans 5(a):**Vat Buzzer Behaviour****Source Code:**

```
// Module (a)
module vat_buzzer_behavior ( output buzzer,
    input above_25_0, above_30_0, low_level_0,
    input above_25_1, above_30_1, low_level_1,
    input select_vat_1 );

    assign buzzer = select_vat_1 ? (low_level_1 | (above_30_1 | ~above_25_1))
        : (low_level_0 | (above_30_0 | ~above_25_0));

endmodule
```

Testbench:

```
// Testbench for module (a) in p5.v
module tb_p5_vat_buzzer_behavior();
    // Mode Declaration
    reg above_25_0, above_30_0, low_level_0, above_25_1, above_30_1, low_level_1, select_vat_1;
    wire buzzer;

    // Instantiate Module
    vat_buzzer_behavior UUT (buzzer, above_25_0, above_30_0, low_level_0, above_25_1, above_30_1, low_level_1, select_vat_1);

    initial begin
        select_vat_1 = 0;
        low_level_0 = 0;
        above_30_0 = 0;
        above_25_0 = 0;
        low_level_1 = 0;
        above_30_1 = 0;
        above_25_1 = 0;

        // Testcase: All possible combinations of input parameters
        repeat(127) begin
            #10;
            select_vat_1 = select_vat_1 ^ (low_level_0 & above_30_0 & above_25_0 & low_level_1 & above_30_1 & above_25_1);
            low_level_0 = low_level_0 ^ (above_30_0 & above_25_0 & low_level_1 & above_30_1 & above_25_1);
            above_30_0 = above_30_0 ^ (above_25_0 & low_level_1 & above_30_1 & above_25_1);
        end
    end
endmodule
```

```


    above_25_0 = above_25_0 ^ (low_level_1 & above_30_1 & above_25_1);
    low_level_1 = low_level_1 ^ (above_30_1 & above_25_1);
    above_30_1 = above_30_1 ^ above_25_1;
    above_25_1 = above_25_1 ^ 1;

end
end

initial begin
    $display("select_vat_1  low_level_0  above_30_0  above_25_0  low_level_1  above_30_1  above_25_1  buzzer
");
    $monitor("      %b          %b          %b          %b          %b          %b          %b          %b"
,select_vat_1,low_level_0,above_30_0,above_25_0,low_level_1,above_30_1,above_25_1,buzzer);
end
endmodule

```

Simulation Waveform

 

Simulation Time: 1280ns

Ans 5(b):**Alarm Priority****Source Code:**

```
// Module (b)
module alarm_priority ( output [2:0] intruder_zone,
                        output valid,
                        input [1:8] zone );

    wire [1:8] winner;

    assign winner[1] = zone[1];
    assign winner[2] = zone[2] & ~zone[1];
    assign winner[3] = zone[3] & ~(zone[2] | zone[1]);
    assign winner[4] = zone[4] & ~(zone[3] | zone[2] | zone[1]);
    assign winner[5] = zone[5] & ~(zone[4] | zone[3] | zone[2] |
    zone[1]);
    assign winner[6] = zone[6] & ~(zone[5] | zone[4] | zone[3] |
    zone[2] | zone[1]);
    assign winner[7] = zone[7] & ~(zone[6] | zone[5] | zone[4] |
    zone[3] | zone[2] | zone[1]);
    assign winner[8] = zone[8] & ~(zone[7] | zone[6] | zone[5] |
    zone[4] | zone[3] | zone[2] |
    zone[1]);
    assign intruder_zone[2] = winner[5] | winner[6] |
    winner[7] | winner[8];
    assign intruder_zone[1] = winner[3] | winner[4] |
    winner[7] | winner[8];
    assign intruder_zone[0] = winner[2] | winner[4] |
    winner[6] | winner[8];

    assign valid = zone[1] | zone[2] | zone[3] | zone[4] |
    zone[5] | zone[6] | zone[7] | zone[8];
endmodule
```

Testbench:

```
// Testbench for module (b) in p5.v
module tb_p5_alarm_priority();
    // Mode Declaration
    wire [2:0] intruder_zone;
    wire valid;
    reg [1:8] zone;

    // Instantiate Module
    alarm_priority DUT (intruder_zo
```

```
ne,valid,zone);
```

```
// Testcase: All possible combinations of input parameters
```

```
initial begin
```

```
    zone = 8'b0;
```

```
    repeat(127) begin
```

```
        #10 zone = zone+1;
```

```
    end
```

```
end
```

```
initial begin
```

```
    $display("zone intruder_zone valid");
```

```
    $monitor(" %d      %d      %d",zone,intruder_zone,valid);
```

```
end
```

```
endmodule
```

Simulated Waveform

	Msgs	
intruder_zone	3'h3	3'h3
valid	1'h1	3'h2
zone	8'h19	8'h19 8'h1a 8'h1b 8'h1c 8'h1d 8'h1e 8'h1f 8'h20 8'h21 8'h22 8'h23 8'h24
Now	1280 ns	260 ns 270 ns 280 ns 290 ns 300 ns 310 ns 320 ns 330 ns 340 ns 350 ns 360 ns 370 ns
Cursor 1	251 ns	251 ns

Waveform shown from **251ns** to **370ns**

Simulation Time: 1280ns

Ans 6:

Model 1 (Decade Counter)

Source Code:

// Given Model

```
module decade_counter ( output reg [3:0] q,  
                        input clk );  
  
    always @(posedge clk)  
        q <= q == 9 ? 0 : q + 1;  
endmodule
```

Note: Since, initial value of the counter is not specified, assume it to be zero

Testbench:

// Testbench for given model


```
module tb_p6_decade_counter();  
    // Mode declaration  
    reg clk;  
    wire [3:0] q;  
  
    // Instantiate given model  
    decade_counter UUT (q,clk);  
  
    initial begin  
        clk = 0;  
        // Assume initial value is zero  
        UUT.q = 4'b0000;  
    end  
  
    always #10 clk = ~clk;  
  
    // Display all parameters  
    initial begin  
        $display("time\t clk q");  
        $monitor("%g\t %b %h",$time,clk,q);  
    end  
endmodule
```

Text Output

VSIM 76> run

#	time	clk	q
# 0	0	0	0
# 10	1	1	1
# 20	0	1	1
# 30	1	2	2
# 40	0	2	2
# 50	1	3	3
# 60	0	3	3
# 70	1	4	4
# 80	0	4	4
# 90	1	5	5
# 100	0	5	5
# 110	1	6	6
# 120	0	6	6
# 130	1	7	7
# 140	0	7	7
# 150	1	8	8
# 160	0	8	8
# 170	1	9	9
# 180	0	9	9
# 190	1	0	0
# 200	0	0	0
# 210	1	1	1

Simulation Waveform

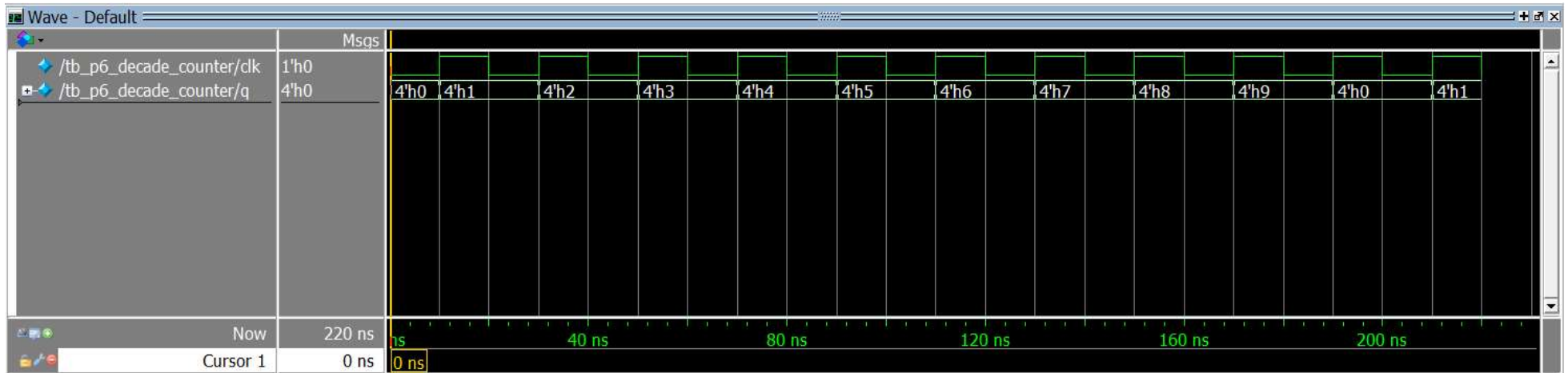

Simulation Time: 210ns

1 Clock Cycle: 10ns

Model 2 (Decoded Counter)

Source Code:

```
// Given Model
module decoded_counter ( output ctrl,
                        input clk );

    reg [3:0] count_value;
    always @(posedge clk)
        count_value <= count_value + 1;

    assign ctrl = count_value == 4'b0111 ||
                count_value == 4'b1011;
endmodule
```

Note: Since, initial value of the counter is not specified, assume it to be zero

Testbench:

```
// Testbench for given model
module tb_p6_decoded_counter();
    // Mode Declaration
    reg clk;
    wire ctrl;
    wire [3:0] count_value;

    // Instantiate given model
    decoded_counter DUT (ctrl,clk);

    assign count_value = DUT.count_value;
    initial begin
        clk = 0;
        // Assume initial value is zero
        DUT.count_value = 4'b0000;
    end


    always #10 clk = ~clk;

    // Display all parameters
    initial begin
        $display("time\t clk count_value ctrl");
        $monitor("%g\t  %b      %d      %b", $time, clk, DUT.count_value, ctrl);
    end
endmodule
```

Text Output

```
VSIM 85> run
# time    clk count_value ctrl
# 0        0      0         0
# 10       1      1         0
# 20       0      1         0
# 30       1      2         0
# 40       0      2         0
# 50       1      3         0
# 60       0      3         0
# 70       1      4         0
# 80       0      4         0
# 90       1      5         0
# 100      0      5         0
# 110      1      6         0
# 120      0      6         0
# 130      1      7         1
# 140      0      7         1
# 150      1      8         0
# 160      0      8         0
# 170      1      9         0
# 180      0      9         0
# 190      1     10         0
# 200      0     10         0
# 210      1     11         1
```

Simulated Waveform:

 


Simulation Time: 220ns

1 Clock Cycle: 10ns

Ans 7:

Circuit Diagram of the Architecture

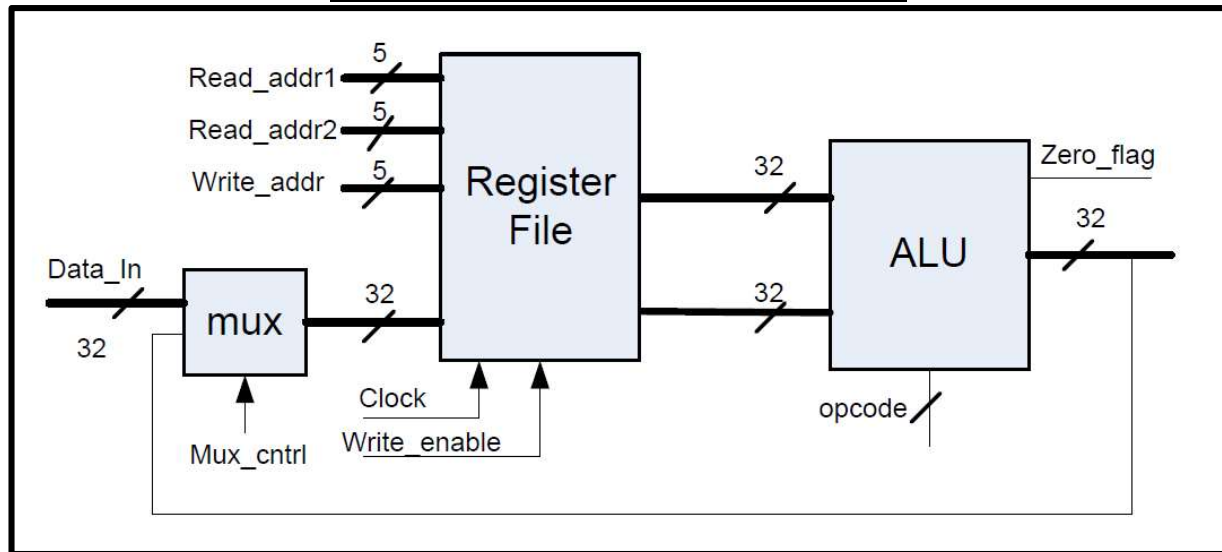

Source Code:

```
// Module for 32x32 Register File
module Register_File (Data_Out_1, Data_Out_2, Data_in, Read_Addr_1, Read_Addr_2, Write_Ad
dr, Write_Enable, Clock);
    // Mode Declaration
    input [31:0] Data_in; // Data to be written
    input [4:0] Read_Addr_1, Read_Addr_2, Write_Addr; // Addresses to Read and Write
    input Write_Enable; // Enable for Write Mode
    input Clock; // Clock
    output [31:0] Data_Out_1, Data_Out_2; // Data to be read from Read_Addr_1
    & Read_Addr_2

    reg [31:0] Reg_File [31:0]; // Memory declaration for 32 32-
    bit Words

    assign Data_Out_1 = Reg_File[Read_Addr_1];
    assign Data_Out_2 = Reg_File[Read_Addr_2];

    always @ (posedge Clock) begin
        if (Write_Enable) begin
            Reg_File[Write_Addr] = Data_in;
        end
    end
endmodule

// Module for ALU
module alu (op, zero_flag, ip0, ip1, opcode);
    // Mode Declaration
```

```

output zero_flag;          // Zero Flag
output [31:0] op;          // ALU Output
input [1:0] opcode;        // ALU Mode of Operation
input [31:0] ip0,ip1;      // ALU Inputs

// opcode :      00          01          10          11
// Operation : Addition      Subtraction      Bitwise AND      Bitwise OR
assign op = opcode[0] ? (opcode[1] ? (ip0&ip1) : (ip0|ip1)) : (opcode[1] ? (ip0-
ip1) : (ip0+ip1));
assign zero_flag = (op == 32'b0);
endmodule

// Module for 2:1 Multiplexer
module mux2_1 (op,ip0,ip1,Mux_cntrl);
output [31:0] op;          // MUX Output
input Mux_cntrl;           // MUX Control Line
input [31:0] ip0,ip1;      // MUX Inputs

// Mux_cntrl :      0          1
// Output : Input 0      Input 1
assign op = Mux_cntrl ? ip1 : ip0;
endmodule

// Module for given Architecture
module p7 (zero_flag, result, Data_in, Read_Addr_1, Read_Addr_2, Write_Addr, Write_Enable
, Mux_cntrl, opcode, Clock);
// Mode Declaration
output zero_flag;
output [31:0] result;
input [31: 0] Data_in;
input [4: 0] Read_Addr_1, Read_Addr_2, Write_Addr;
input Mux_cntrl, Write_Enable, Clock;
input [1:0] opcode;

wire [31:0] mux_OP, Data_Out_1, Data_Out_2, result;

// Import Modules for all blocks
/*      Module      | Name of      |      Parameters
*              | Instance |
-----*/
mux2_1      MUX      (mux_OP,Data_in,result,Mux_cntrl);
Register_File regFile (Data_Out_1, Data_Out_2, mux_OP, Read_Addr_1, Read_Addr_2,
Write_Addr, Write_Enable, Clock);
alu      ALU      (result,zero_flag,Data_Out_1,Data_Out_2,opcode);
endmodule

```

Test Bench:

```
// Testbench for p7 module in p7.v
module tb_p7 ();
    // Mode Declarations
    // All terms explained in p7.v
    wire zero_flag;
    wire [31:0] result;
    reg [31:0] Data_in;
    reg [4:0] Read_Addr_1, Read_Addr_2, Write_Addr;
    reg Write_Enable, Mux_cntrl, Clock = 0;
    reg [1:0] opcode;

    always #1 Clock = ~Clock;

    // Instantiate p7
    p7 DUT_p7 (zero_flag, result, Data_in, Read_Addr_1, Read_Addr_2, Write_Addr, Write_Enable, Mux_cntrl, opcode, Clock);

    wire [31:0] sum, mux_OP;
    assign sum = DUT_p7.regFile.Reg_File[31]; // Value Stored at register 31 (Sum of input Data)
    assign mux_OP = DUT_p7.mux_OP; // Output of 2:1 Multiplexer
    assign Data_Out_1 = DUT_p7.Data_Out_1; // Data Output 1 from Register File
    assign Data_Out_2 = DUT_p7.Data_Out_2; // Data Output 2 from Register File

    integer i;
    initial begin
        // Write Data to Register File
        Mux_cntrl = 0;
        Write_Enable = 1;
        for(i = 0; i < 25; i = i+1) begin
            #2;
            Write_Addr = i;
            Data_in = $urandom%(64);
        end
        // Initialize register 31 to zero to avoid garbage values
        #2;
        Write_Addr = 31;
        Data_in = 31'b0;
        // Calculate Sum of data in registers 0 to 24
        #2;
        Data_in = 31'bx;
        Mux_cntrl = 1;
        Read_Addr_1 = 31;
        Read_Addr_2 = 31;
    end
endmodule
```



```

opcode = 0;

for (i = 0; i < 25; i = i+1) begin
    #2 Read_Addr_1 = i;
end
end


// Display all Parameters
initial begin
    $monitor("time=%g\tMux_cntrl=%b\tData_in=%d\tmux_OP=%d\tRead_Addr_1=%d\tRead_Addr_2=%d\tWrite_Enable=%b\tWrite_Addr=%d\tData_Out_1=%d\tData_Out_2=%d\topcode=%b\tSum=%d",
    $time,Mux_cntrl,Data_in,mux_OP,Read_Addr_1,Read_Addr_2,Write_Enable,Write_Addr,Data_Out_1,Data_Out_2,opcode,sum);
end
endmodule

```

Simulated Waveforms:

(1 Clock Cycle = 1ns)

Writing Data to Register File

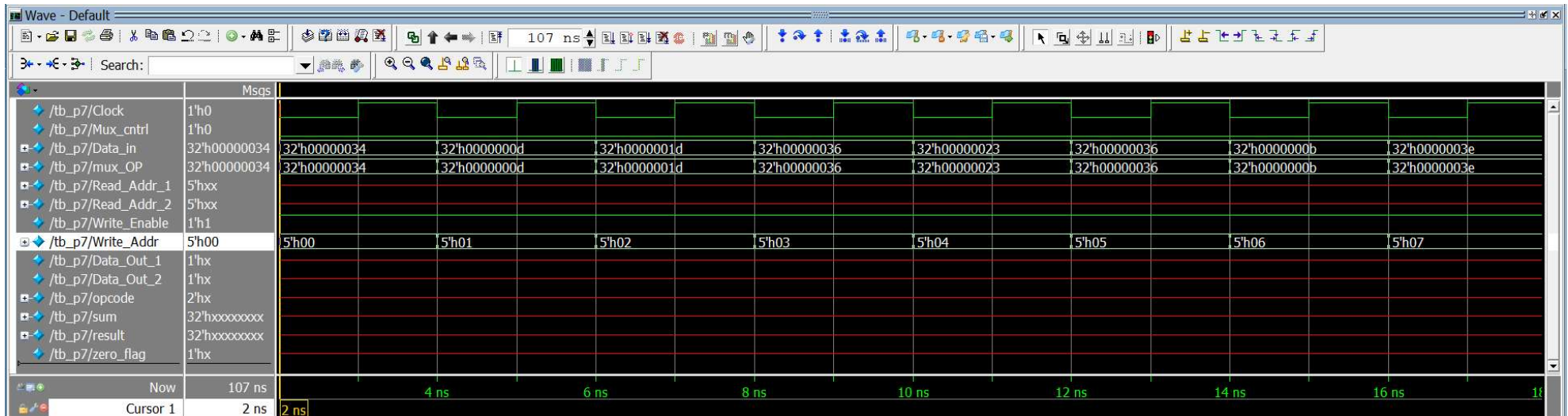

Simulation Time: 2ns to 18ns

Initialize Register 31 to zero to avoid garbage values:

	Msgs	
/tb_p7/Clock	1'h0	
/tb_p7/Mux_cntrl	1'h0	
/tb_p7/Data_in	32'h00000034	32'h00000000
/tb_p7/mux_OP	32'h00000034	32'h00000000
/tb_p7/Read_Addr_1	5'hxx	
/tb_p7/Read_Addr_2	5'hxx	
/tb_p7/Write_Enable	1'h1	
/tb_p7/Write_Addr	5'h00	5'h1f
/tb_p7/Data_Out_1	1'hx	
/tb_p7/Data_Out_2	1'hx	
/tb_p7/opcode	2'hx	
/tb_p7/sum	32'hxxxxxxxx	32'h00000000
/tb_p7/result	32'hxxxxxxxx	
/tb_p7/zero_flag	1'hx	
Now	107 ns	54 ns
Cursor 1	2 ns	

Simulation Time: 52ns to 54ns

Calculate Sum of Data in Registers 0 to 24:

	Msgs						
/tb_p7/Clock	1'h0						
/tb_p7/Mux_cntrl	1'h0						
/tb_p7/Data_in	32'h00000034	32'hxxxxxxxx					
/tb_p7/mux_OP	32'h00000034	32'h00000341	32'h00000314	32'h0000031b	32'h0000032d	32'h00000346	32'h0000033f
/tb_p7/Read_Addr_1	5'hxx	5'h15	5'h16		5'h17		5'h18
/tb_p7/Read_Addr_2	5'hxx	5'h1f					
/tb_p7/Write_Enable	1'h1						
/tb_p7/Write_Addr	5'h00	5'h1f					
/tb_p7/Data_Out_1	1'hx						
/tb_p7/Data_Out_2	1'hx						
/tb_p7/opcode	2'hx	2'h0					
/tb_p7/sum	32'hxxxxxxxx	32'h0000030d	32'h00000314		32'h0000032d		32'h0000033f
/tb_p7/result	32'hxxxxxxxx	32'h00000341	32'h00000314	32'h0000031b	32'h0000032d	32'h00000346	32'h0000033f
/tb_p7/zero_flag	1'hx						32'h00000351
Now	107 ns	100 ns	102 ns		104 ns		106 ns
Cursor 1	2 ns						

Simulation Time: 98ns to 108ns